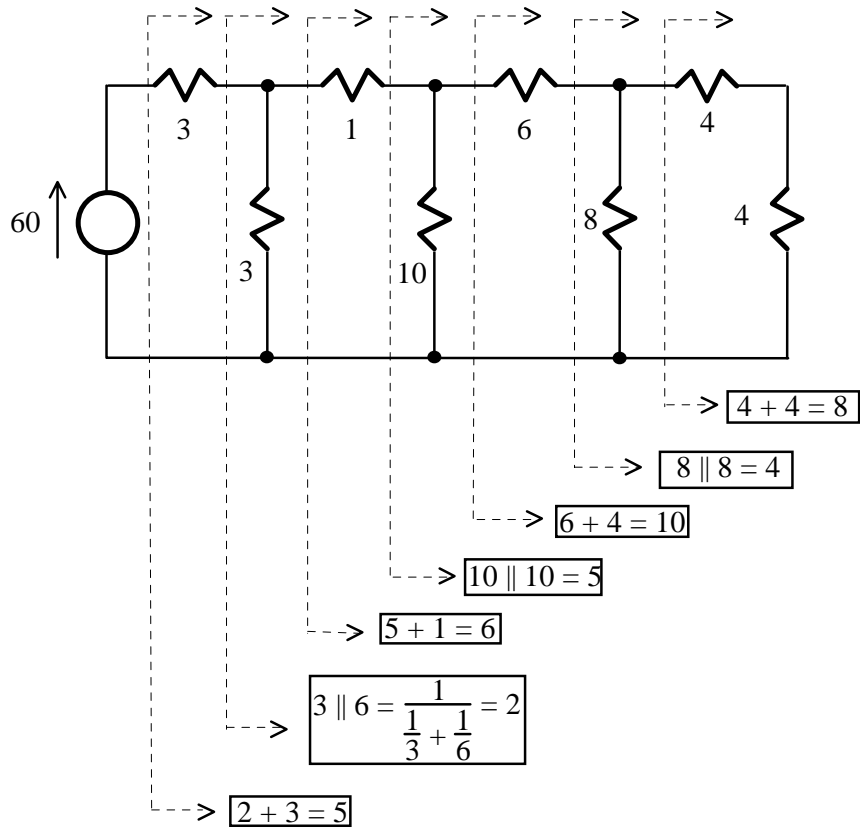


F.3 Analiza Cir EI c.c. I


Q.1

Source current




$$\text{Source current} = \frac{60}{5} = 12 \text{ A}$$

Value for i



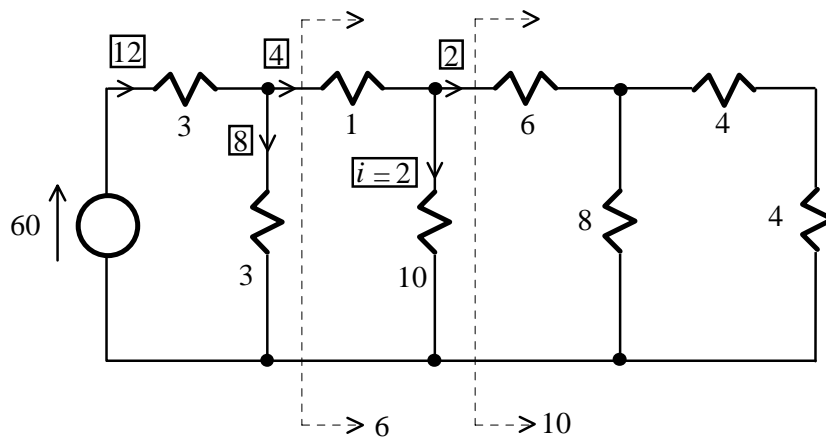


Q.2

Original circuit

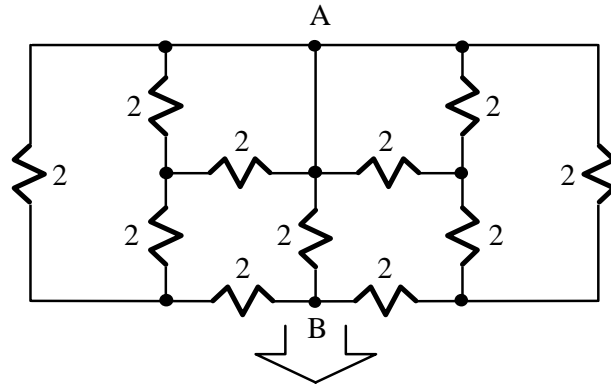


All units in
V, A, Ω

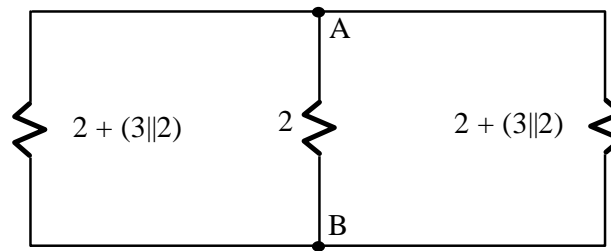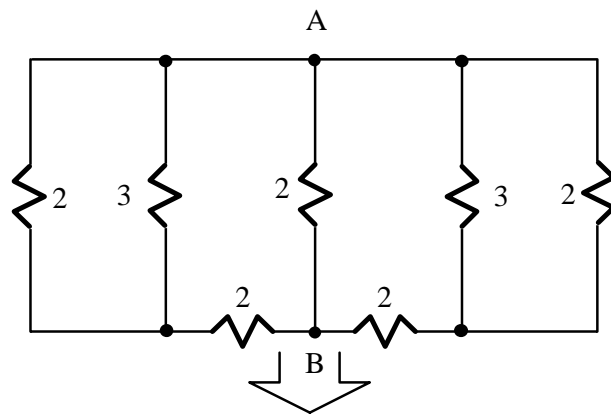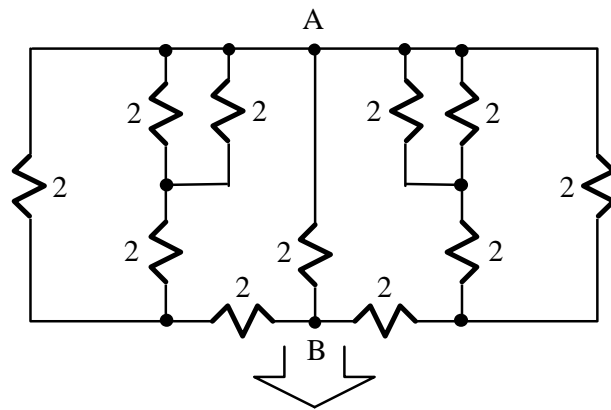

$$2 + (3||2) = 2 + \frac{1}{\frac{1}{3} + \frac{1}{2}} = 2 + \frac{6}{5} = 3.2$$



$$\text{Equivalent resistance} = 2 \parallel 3.2 \parallel 3.2 = 2 \parallel 1.6 = \frac{1}{0.5 + 0.625} = 0.889 \Omega$$

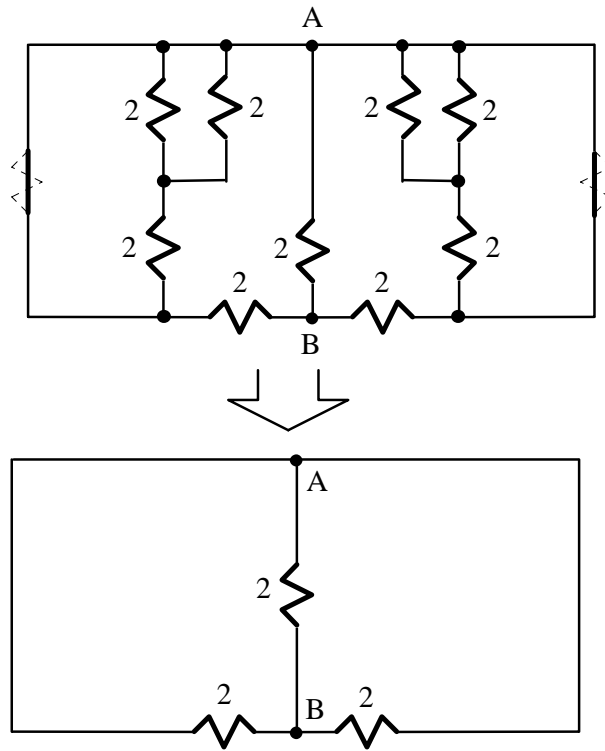When outer two resistors are short-circuited



$$\text{Equivalent resistance} = 2 \parallel 2 \parallel 2 = \frac{2}{3} = 0.666 \Omega$$

Q.3 Mesh analysis

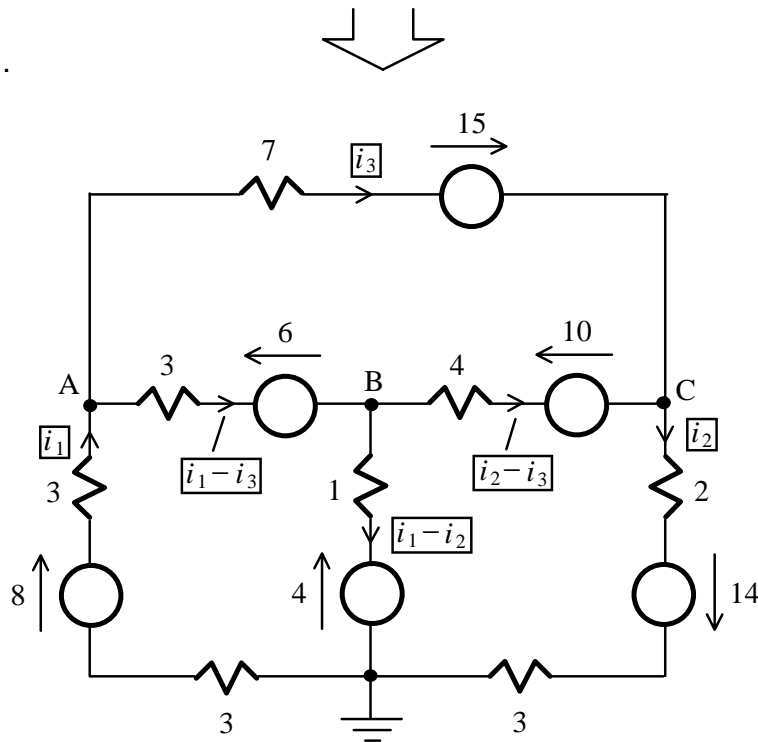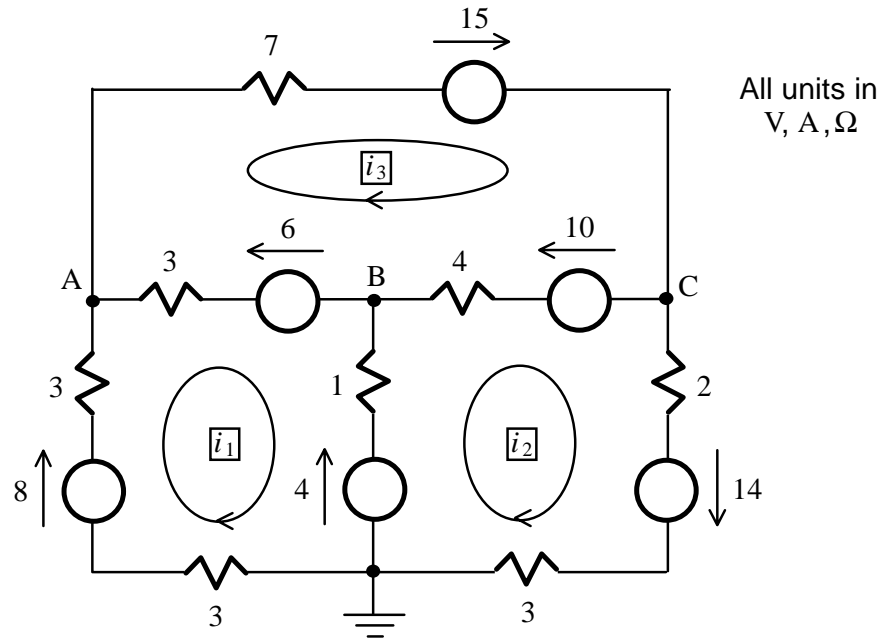

Applying KVL for the three loops shown:

$$8 - 3i_1 - 3(i_1 - i_3) - 6 + (i_1 - i_2) - 4 - 3i_1 = 0$$

$$14 - 3i_2 + 4 - (i_2 - i_1) - 4(i_2 - i_3) - 10 - 2i_2 = 0$$

$$15 + 10 - 4(i_3 - i_2) + 6 - 3(i_3 - i_1) - 7i_3 = 0$$

Simplifying:

$$-2 = 10i_1 - i_2 - 3i_3$$

$$8 = -i_1 + 10i_2 - 4i_3$$

$$31 = -3i_1 - 4i_2 + 14i_3$$

In matrix form:

$$\begin{bmatrix} 10 & -1 & -3 \\ -1 & 10 & -4 \\ -3 & -4 & 14 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} -2 \\ 8 \\ 31 \end{bmatrix}$$

Solving (actually not required in this question):

$$-2 + 10(8) = 10i_1 - i_2 - 3i_3 + 10(-i_1 + 10i_2 - 4i_3) \Rightarrow 78 = 99i_2 - 43i_3$$


$$31 - 3(8) = -3i_1 - 4i_2 + 14i_3 - 3(-i_1 + 10i_2 - 4i_3) \Rightarrow 7 = -34i_2 + 26i_3$$

$$26(78) + 43(7) = 26(99i_2 - 43i_3) + 43(-34i_2 + 26i_3) \Rightarrow i_2 = \frac{26(78) + 43(7)}{26(99) - 43(34)} = \frac{2329}{1112}$$

$$34(78) + 99(7) = 34(99i_2 - 43i_3) + 99(-34i_2 + 26i_3) \Rightarrow i_3 = \frac{34(78) + 99(7)}{-34(43) + 99(26)} = \frac{3345}{1112}$$

$$i_1 = -8 + 10i_2 - 4i_3 = -8 + \frac{23290}{1112} - \frac{4(3345)}{1112} = \frac{1014}{1112}$$

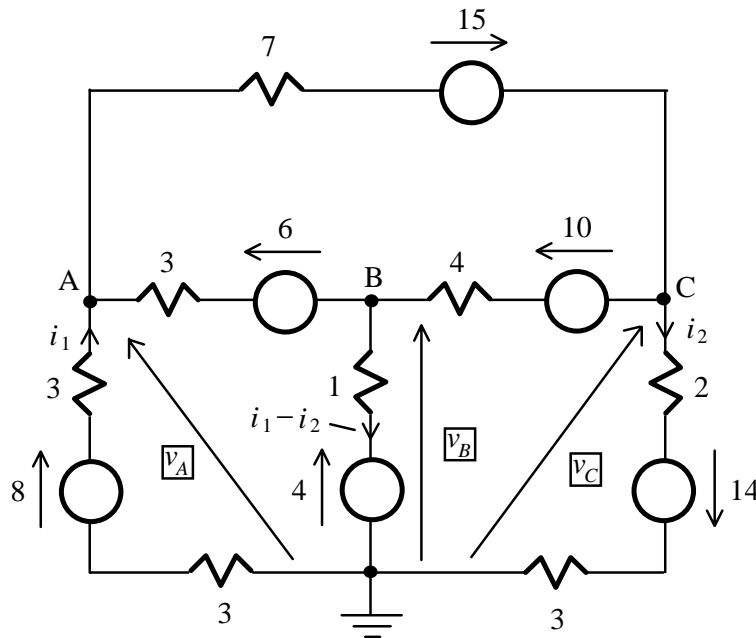Voltages of nodes A, B and C with respect to ground:




$$v_A = 8 - 6i_1$$

$$v_B = 4 + i_1 - i_2$$

$$v_C = -14 + 5i_2$$

Nodal analysis

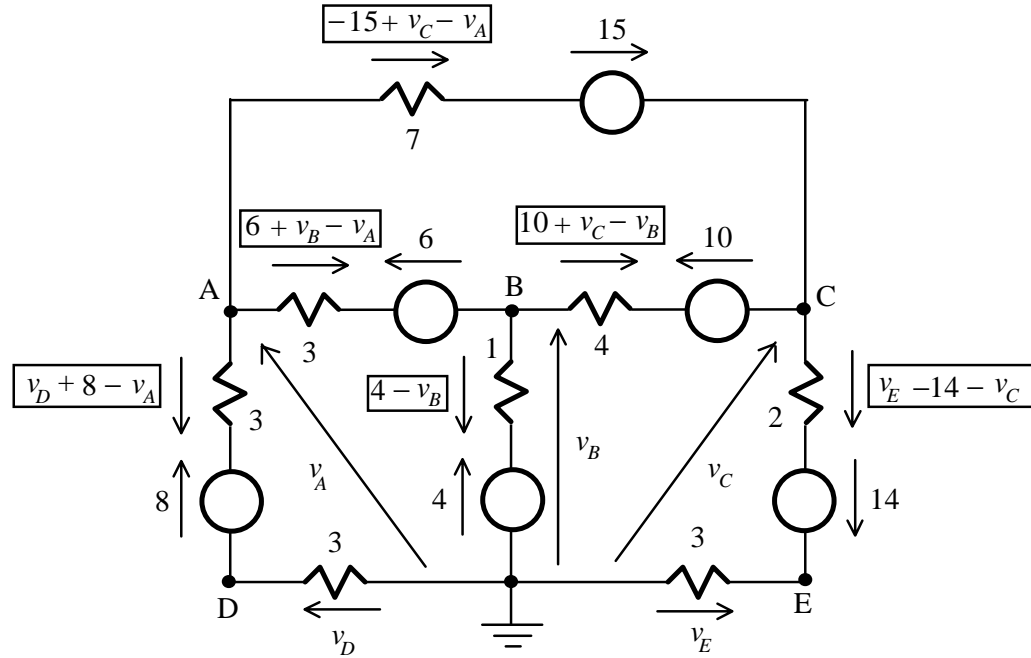

Applying KCL to nodes A, B, C, D and E:

$$\frac{v_D + 8 - v_A}{3} + \frac{6 + v_B - v_A}{3} + \frac{v_C - v_A - 15}{7} = 0$$

$$\frac{4 - v_B}{1} + \frac{v_A - v_B - 6}{3} + \frac{v_C - v_B + 10}{4} = 0$$

$$\frac{v_E - 14 - v_C}{2} + \frac{v_A - v_C + 15}{7} + \frac{v_B - v_C - 10}{4} = 0$$

$$\frac{v_D + 8 - v_A}{3} + \frac{v_D}{3} = 0$$


$$\frac{v_E - 14 - v_C}{2} + \frac{v_E}{3} = 0$$

In matrix form:

$$\begin{bmatrix} \frac{1}{3} + \frac{1}{3} + \frac{1}{7} & -\frac{1}{3} & -\frac{1}{7} & -\frac{1}{7} & 0 \\ -\frac{1}{3} & 1 + \frac{1}{3} + \frac{1}{4} & -\frac{1}{4} & 0 & 0 \\ -\frac{1}{7} & -\frac{1}{4} & \frac{1}{2} + \frac{1}{7} + \frac{1}{4} & 0 & -\frac{1}{2} \\ \frac{1}{3} & 0 & 0 & -\frac{1}{3} - \frac{1}{3} & 0 \\ 0 & 0 & \frac{1}{2} & 0 & -\frac{1}{2} - \frac{1}{3} \end{bmatrix} \begin{bmatrix} v_A \\ v_B \\ v_C \\ v_D \\ v_E \end{bmatrix} = \begin{bmatrix} \frac{8}{3} + \frac{6}{3} - \frac{15}{7} \\ \frac{1}{4} - 2 + \frac{10}{4} \\ -7 + \frac{15}{7} - \frac{10}{4} \\ \frac{8}{3} \\ -\frac{14}{2} \end{bmatrix}$$

$$\begin{bmatrix} \frac{1}{3} + \frac{1}{3} + \frac{1}{7} & & & & & \\ & -\frac{1}{3} & & & & \\ & 1 + \frac{1}{3} + \frac{1}{4} & & & & \\ & & \frac{1}{2} + \frac{1}{7} + \frac{1}{4} & & & \\ & & & -\frac{1}{3} - \frac{1}{3} & & \\ & & & & -\frac{1}{2} - \frac{1}{3} & \end{bmatrix} \begin{bmatrix} v_A \\ v_B \\ v_C \\ v_D \\ v_E \end{bmatrix} = \begin{bmatrix} \frac{8}{3} + \frac{6}{3} - \frac{15}{7} \\ \frac{1}{4} - 2 + \frac{10}{4} \\ -7 + \frac{15}{7} - \frac{10}{4} \\ \frac{8}{3} \\ -\frac{14}{2} \end{bmatrix}$$

Q.4

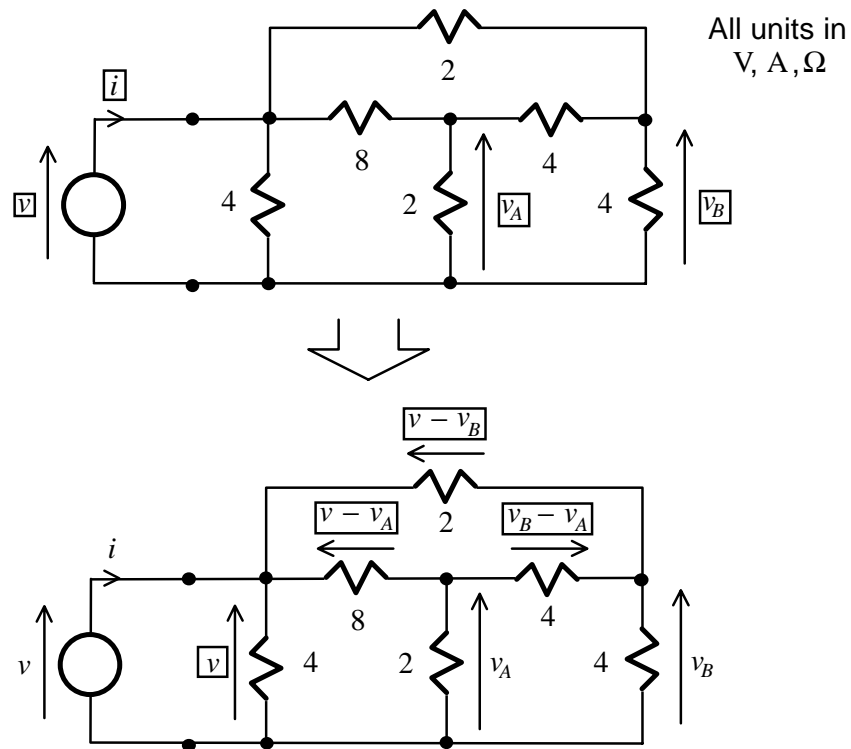

Applying KCL:

$$i = \frac{v}{4} + \frac{v - v_A}{8} + \frac{v - v_B}{2}$$

$$\frac{v_A}{2} + \frac{v_A - v}{8} + \frac{v_A - v_B}{4} = 0 \Rightarrow 4v_A + v_A - v + 2v_A - 2v_B = 7v_A - 2v_B - v = 0$$

$$\frac{v_B}{4} + \frac{v_B - v_A}{4} + \frac{v_B - v}{2} = 0 \Rightarrow v_B + v_B - v_A + 2v_B - 2v = -v_A + 4v_B - 2v = 0$$

Eliminating v_A and v_B :

$$(7v_A - 2v_B - v) + 7(-v_A + 4v_B - 2v) = 0 \Rightarrow 26v_B - 15v = 0 \Rightarrow v_B = \frac{15}{26}v$$

$$2(7v_A - 2v_B - v) + (-v_A + 4v_B - 2v) = 0 \Rightarrow 13v_A - 4v = 0 \Rightarrow v_A = \frac{4}{13}v$$

$$i = \frac{v}{4} + \frac{v-v_A}{8} + \frac{v-v_B}{2} = \left(\frac{1}{4} + \frac{1}{8} + \frac{1}{2}\right)v - \frac{1}{8}\left(\frac{4}{13}\right)v - \frac{1}{2}\left(\frac{15}{26}\right)v = \frac{57}{104}v$$

The equivalent resistance without the 13Ω resistor is therefore


$$\frac{v}{i} = \frac{104}{57} = 1.82\Omega$$

and the equivalent resistance with the 13Ω series resistor is

$$\text{Equivalent resistance} = 14.82\Omega$$

Q.5


Equivalent resistance

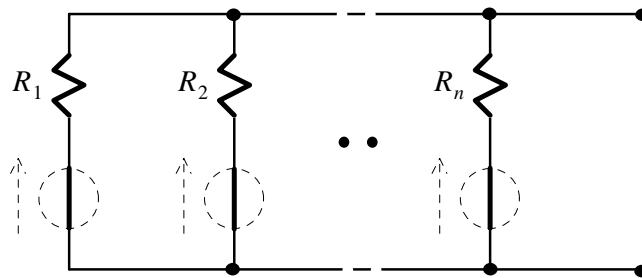

Since the resistors are in parallel, the equivalent resistance R is

$$\frac{1}{R} = \frac{1}{R_1} + \dots + \frac{1}{R_n}$$


Short circuit current

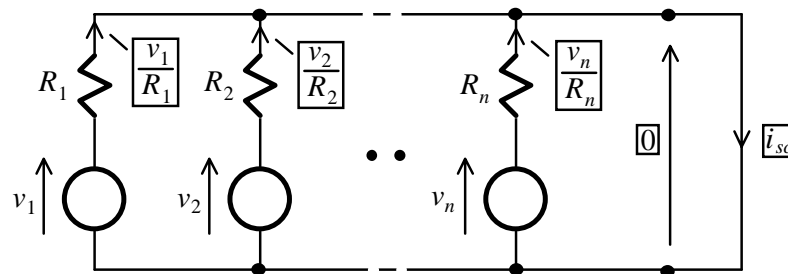

Applying KCL:

$$i_{sc} = \frac{v_1}{R_1} + \dots + \frac{v_n}{R_n}$$


Norton's equivalent circuit

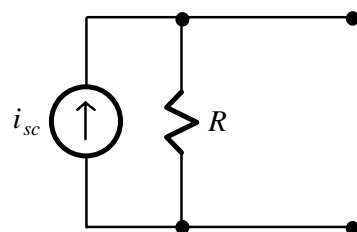

$$\frac{1}{R} = \frac{1}{R_1} + \dots + \frac{1}{R_n}$$

$$i_{sc} = \frac{v_1}{R_1} + \dots + \frac{v_n}{R_n}$$


Thevenin's equivalent circuit

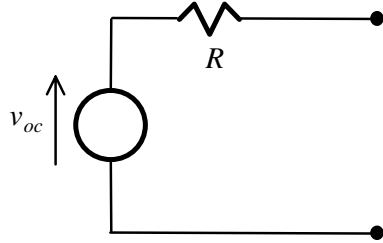

$$\frac{1}{R} = \frac{1}{R_1} + \dots + \frac{1}{R_n}$$


$$v_{oc} = Ri_{sc} = \frac{\frac{v_1}{R_1} + \dots + \frac{v_n}{R_n}}{\frac{1}{R_1} + \dots + \frac{1}{R_n}}$$

Q.6 Re-drawing original circuit

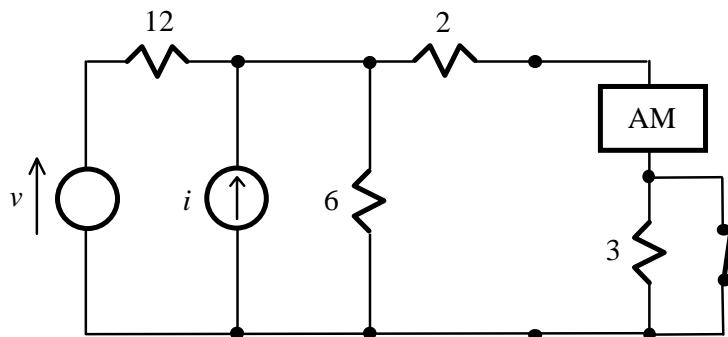


All units in V, A, Ω

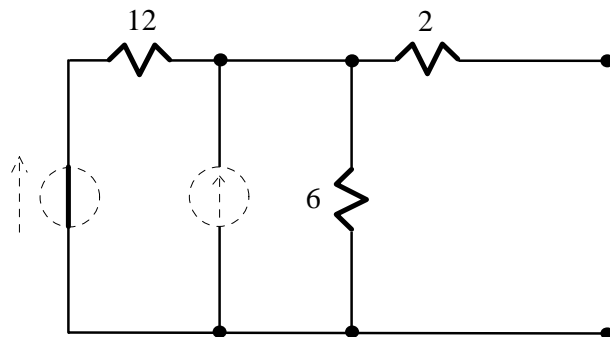Equivalent resistance without $3\ \Omega$ resistor



$$\text{Equivalent resistance } R = 2 + (6 \parallel 12) = 2 + \frac{1}{\frac{1}{6} + \frac{1}{12}} = 2 + 4 = 6\ \Omega$$


Using Norton's equivalent circuit

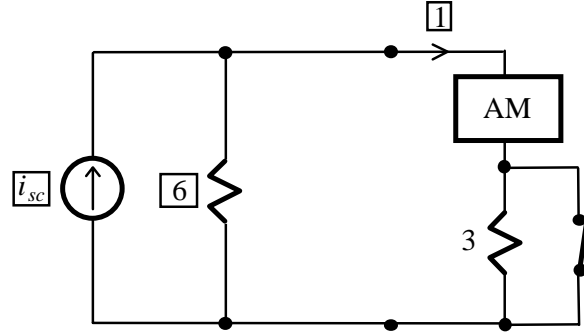

Since AM reads 1A


$$i_{sc} = 1A$$

Thus, when the switch is open

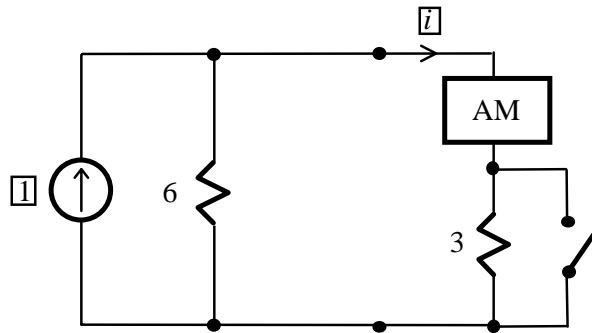

$$i = 1 \times \left(\frac{6}{6+3} \right) = \frac{2}{3} A$$

Q.7

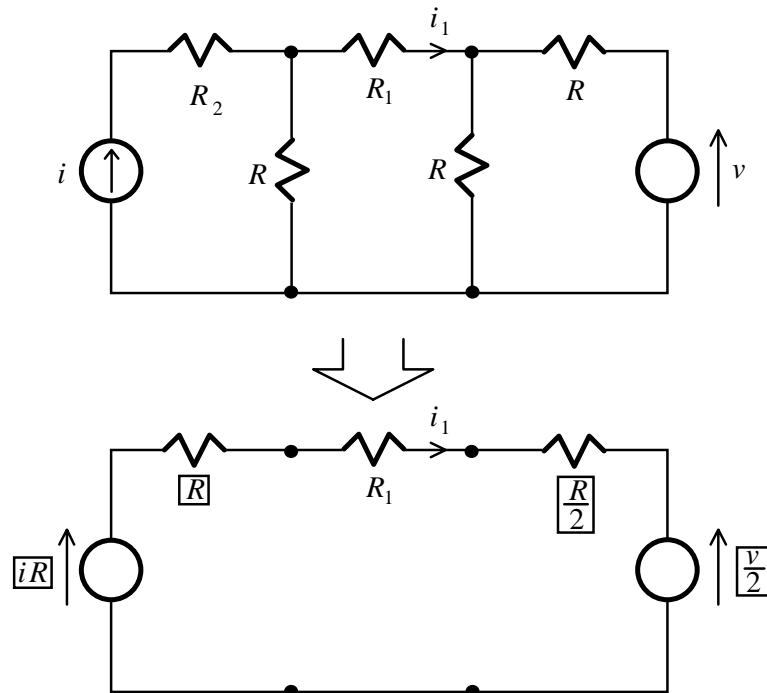


$$i_1 = \frac{iR - \frac{v}{2}}{\frac{3R}{2} + R_1} = \frac{2iR - v}{3R + 2R_1}$$

F.4 Analiza Cir EI c.c. II

Q.1


Load current due to Battery 1

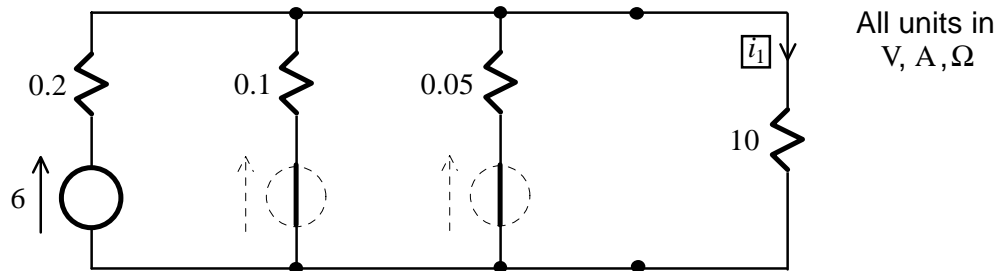

$$\text{Current from source} = \frac{6}{0.2 + 0.1 \parallel 0.05 \parallel 10} = \frac{6}{0.2 + \frac{1}{\frac{1}{10+20} + 0.1}} = \frac{6}{0.2 + 0.033} = 25.75$$

$$i_1 = 25.75 \times \left(\frac{0.1 \parallel 0.05}{10 + 0.1 \parallel 0.05} \right) = 25.75 \times \left(\frac{\frac{1}{\frac{1}{10+20}}}{10 + \frac{1}{\frac{1}{10+20}}} \right) = 25.75 \times \left(\frac{0.033}{10.033} \right) = 0.0847 \text{ A}$$


Load current due to Battery 2

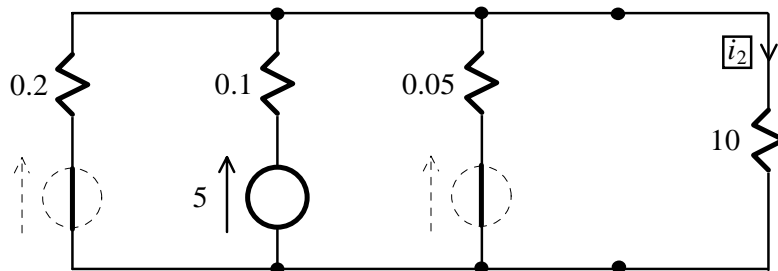

$$\text{Current from source} = \frac{5}{0.1 + 0.2 \parallel 0.05 \parallel 10} = \frac{5}{0.1 + \frac{1}{\frac{1}{5+20} + 0.1}} = \frac{5}{0.1 + 0.04} = 35.71$$

$$i_2 = 35.71 \times \left(\frac{0.2 \parallel 0.05}{10 + 0.2 \parallel 0.05} \right) = 35.71 \times \left(\frac{\frac{1}{\frac{1}{5+20}}}{10 + \frac{1}{\frac{1}{5+20}}} \right) = 35.71 \times \left(\frac{0.04}{10.04} \right) = 0.1423 \text{ A}$$

Load current due to Battery 3

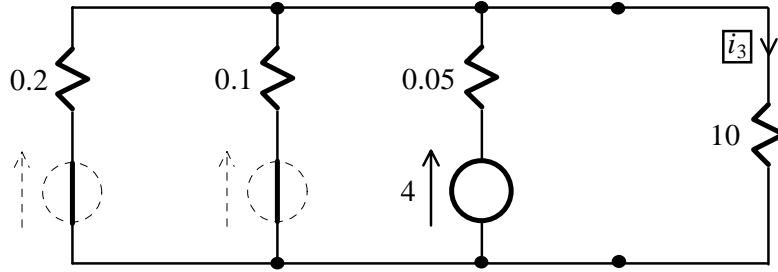

$$\text{Current from source} = \frac{4}{0.05 + 0.2 \parallel 0.1 \parallel 10} = \frac{4}{0.05 + \frac{1}{5+10+0.1}} = \frac{4}{0.05 + 0.066} = 34.48$$


$$i_3 = 34.48 \times \left(\frac{0.2 \parallel 0.1}{10 + 0.2 \parallel 0.1} \right) = 34.48 \times \left(\frac{\frac{1}{5+10}}{10 + \frac{1}{5+10}} \right) = 34.48 \times \left(\frac{0.067}{10.07} \right) = 0.2294 \text{ A}$$

Actual load current

$$i = i_1 + i_2 + i_3 = 0.0847 + 0.1423 + 0.2294 = 0.4564 \text{ A}$$

Q.2

Current due to 25V voltage source

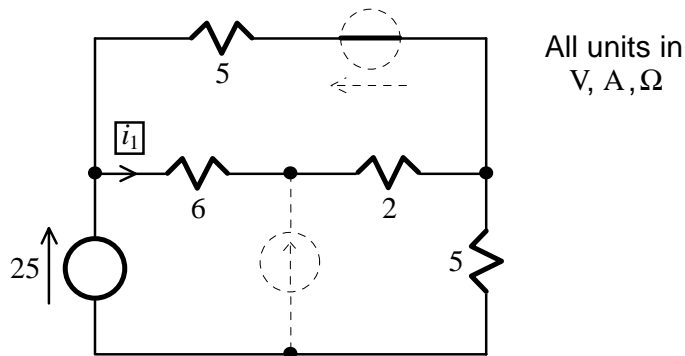


All units in V, A, Ω

$$\text{Current from source} = \frac{25}{5 + 5 \parallel (6+2)} = \frac{25}{5 + \frac{1}{\frac{1}{5} + \frac{1}{8}}} = \frac{25}{5 + 3.08} = 3.09$$

$$i_1 = 3.09 \left(\frac{5}{5+8} \right) = 1.19 \text{ A}$$


Current due to 20V voltage source

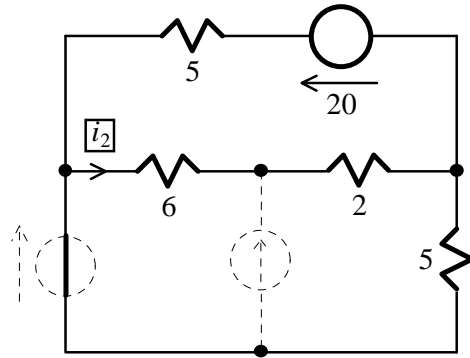

$$\text{Current from source} = \frac{20}{5 + 5 \parallel (6+2)} = \frac{20}{5 + \frac{1}{\frac{1}{5} + \frac{1}{8}}} = \frac{20}{5 + 3.08} = 2.48$$

$$i_2 = 2.48 \left(\frac{5}{5+8} \right) = 0.954 \text{ A}$$

Current due to current source

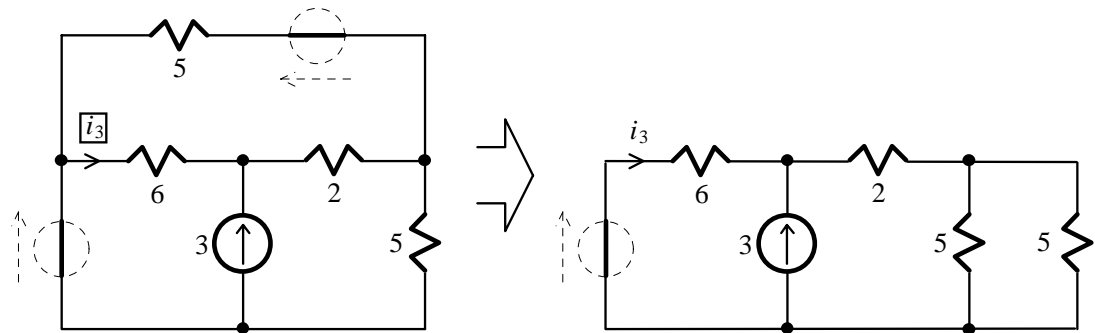


$$i_3 = -3 \left[\frac{2 + (5 \parallel 5)}{6 + 2 + (5 \parallel 5)} \right] = -3 \left[\frac{2 + \frac{1}{0.2+0.2}}{8 + \frac{1}{0.2+0.2}} \right] = -1.286 \text{ A}$$

Actual current

$$i = i_1 + i_2 + i_3 = 1.19 + 0.954 - 1.286 = 0.858 \text{ A}$$

Q.3

Open circuit voltage

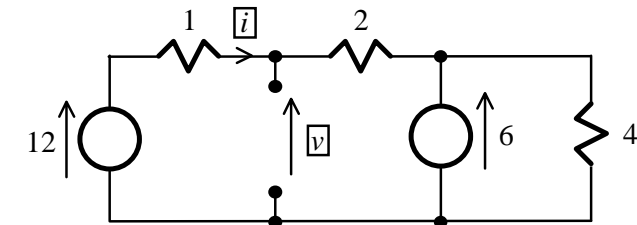


All units in V, A, Ω

$$i = \frac{12 - 6}{1 + 2} = 2$$


$$v = 12 - i = 10 \text{ V}$$

Equivalent resistance

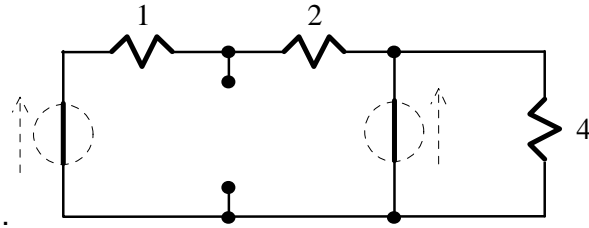


$$\text{Resistance across terminals} = 1 \parallel 2 = \frac{1}{1 + \frac{1}{2}} = 0.667 \Omega$$

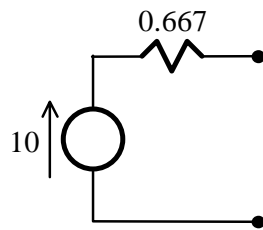Thevenin's equivalent circuit and maximum power




$$\text{Maximum power transferable (with a } 0.667 \Omega \text{ load)} = \left(\frac{10}{2 \times 0.667} \right)^2 0.667 = 37.5 \text{ W}$$

Q.4

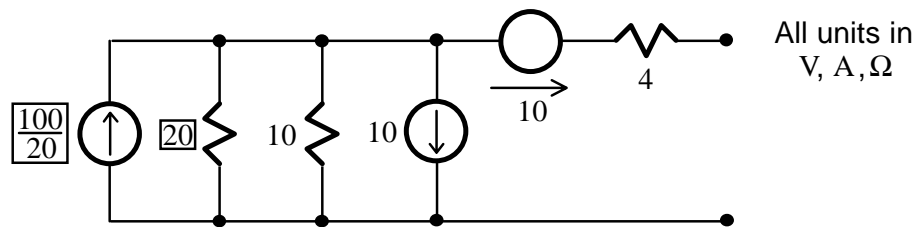

$$\text{Combined current of current sources} = 10 - \frac{100}{20} = 5$$
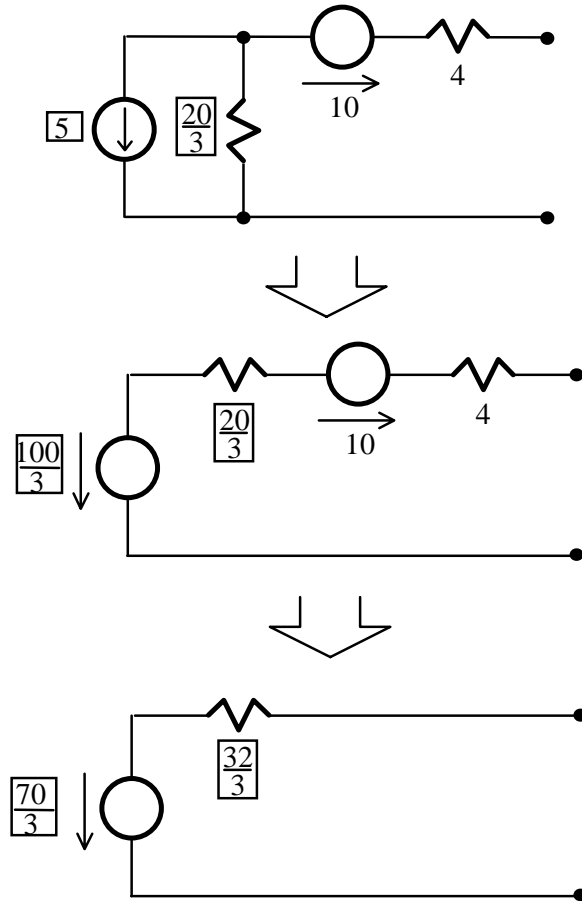
$$\text{Equivalent parallel resistance} = 20 \parallel 10 = \frac{1}{\frac{1}{20} + \frac{1}{10}} = \frac{20}{3}$$




Resistor that draws $2\text{ A} = \frac{70}{3 \times 2} - \frac{32}{3} = 1\Omega$

Resistor that absorbs the maximum power = $\frac{32}{3}\Omega$

Maximum power that can be transferred = $\left(\frac{70}{3} \parallel \frac{32 \times 2}{3}\right)^2 \frac{32}{3} = \frac{1225}{96}\text{ W}$

Q.5

Thevenin's equivalent circuit

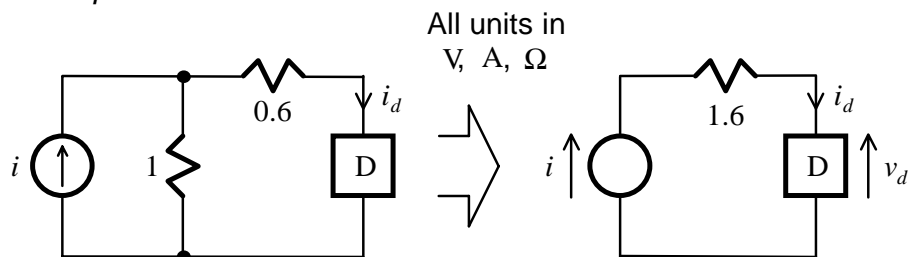


Device current given $i = 1.6\text{ A}$

Applying KVL:

$$i = 1.6i_d + v_d = 1.6$$

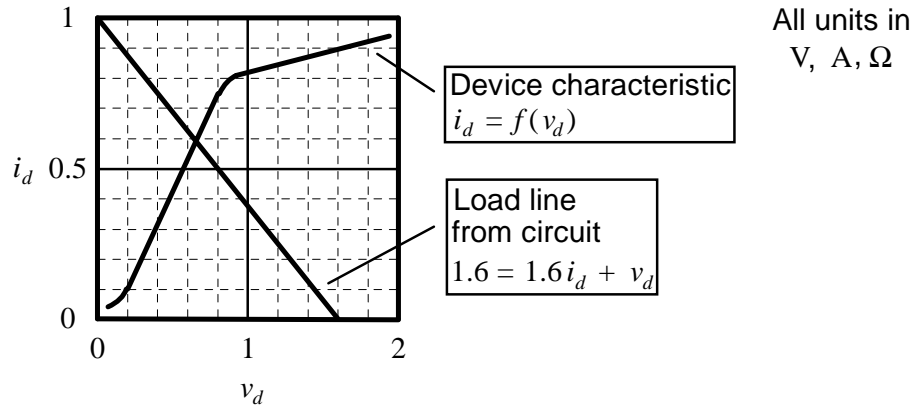
v_d and i_d can be found from solving this (which gives rise to the load line) and the relationship $i_d = f(v_d)$ given by the characteristic curve. Specifically, when $i_d = 0$, $v_d = 1.6$. Also, when $v_d = 0$, $i_d = 1$.



The point of intersection gives


$$i_d = 0.6 \text{ A}$$

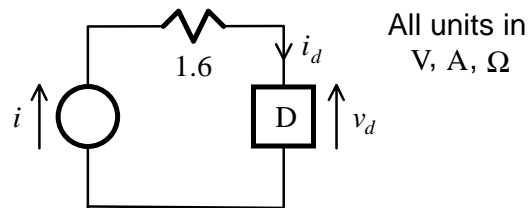Source current for power dissipated in D to be 0.6W



$$\text{Power dissipated in D} = i_d v_d = 0.6$$

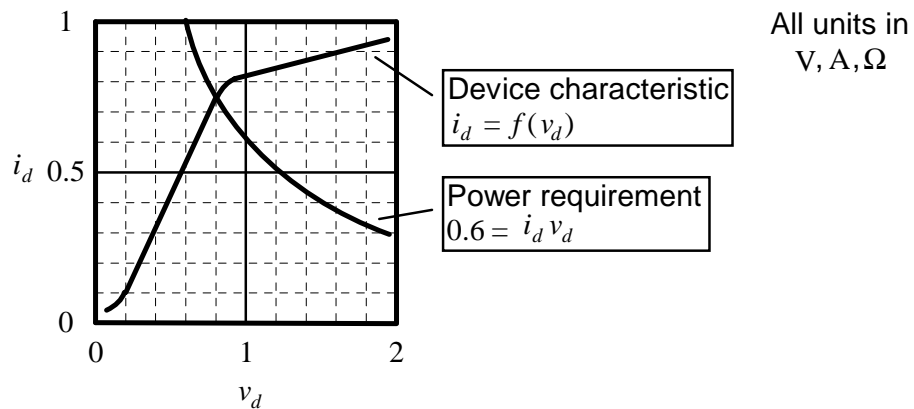The device voltage and current can be found from solving this and the relationship $i_d = f(v_d)$ given by the characteristic curve:



The point of intersection gives

$$v_d \approx 0.8 \text{ V}$$

$$i_d \approx 0.75 \text{ A}$$

From KVL:

$$i = 1.6i_d + v_d \approx 1.6(0.75) + 0.8 = 2 \text{ A}$$

Q.6

Voltage gain

Applying KCL to the second half of the circuit:

$$v_2 = -20(50i_1) = -1000i_1$$

Applying KVL to the first half of the circuit:

$$v_1 = 2i_1 + \frac{v_2}{5000}$$

Eliminating i_1 :

$$v_1 = -2\left(\frac{v_2}{1000}\right) + \frac{v_2}{5000} = \frac{-1.8v_2}{1000} \Rightarrow v_2 = -\frac{1000}{1.8}v_1$$

The voltage gain is


$$\frac{v_2}{v_1} = -\frac{1000}{1.8}$$

The gain in voltage magnitudes is

$$\left|\frac{v_2}{v_1}\right| = \frac{1000}{1.8} = 20\log\left(\frac{1000}{1.8}\right)\text{dB} = 55\text{dB}$$

Equivalent resistance

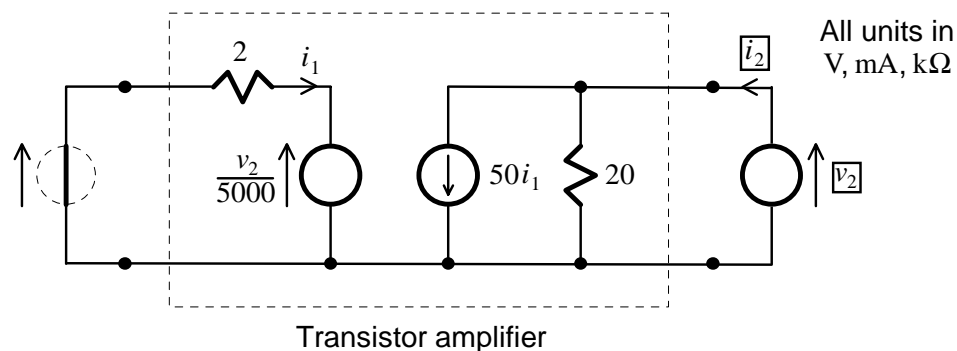To determine the equivalent resistance as seen from the output terminals, all independent sources have to be replaced by their internal resistances and a voltage source has to be applied to these two terminals:



$$-2i_1 = \frac{v_2}{5000}$$

$$i_2 = 50i_1 + \frac{v_2}{20} = -50\left(\frac{v_2}{10000}\right) + \frac{v_2}{20} = \frac{9v_2}{200}$$

$$\text{Equivalent resistance} = \frac{v_2}{i_2} = \frac{200}{9} \text{ k}\Omega$$

Note that in calculating this resistance or in using superposition, dependent sources must not be replaced by their internal resistances.

Thevenin's equivalent circuit

