

F.5 Analiza Cir El c.a. I

Q.1	(a)	(b)
AC waveform	$5\sqrt{2} \sin(\omega t)$ $= 5\sqrt{2} \cos\left(\omega t - \frac{\pi}{2}\right)$ $= \operatorname{Re}\left[\left(5e^{-j\pi/2}\right)\left(\sqrt{2}e^{j\omega t}\right)\right]$	$5\sqrt{2} \cos(\omega t)$ $= \operatorname{Re}\left[\left(5e^{j0}\right)\left(\sqrt{2}e^{j\omega t}\right)\right]$
Peak value	$5\sqrt{2}$	$5\sqrt{2}$
Frequency	$\omega \text{ rad/s} = \frac{\omega}{2\pi} \text{ Hz}$	$\omega \text{ rad/s} = \frac{\omega}{2\pi} \text{ Hz}$
RMS value	5	5
Phase	$-\frac{\pi}{2} = -90^\circ$	0
Phasor	$5 e^{-j\pi/2} = 5 \angle -90^\circ$	$5 e^{j0} = 5 \angle 0^\circ = 5$

	(c)	(d)
AC waveform	$10\sqrt{2} \sin(20t + 30^\circ)$ $= 10\sqrt{2} \cos(20t - 60^\circ)$ $= \operatorname{Re}\left[\left(10e^{-j\pi/3}\right)\left(\sqrt{2}e^{j20t}\right)\right]$	$120\sqrt{2} \cos(314t - 45^\circ)$ $= \operatorname{Re}\left[\left(120e^{-j\pi/4}\right)\left(\sqrt{2}e^{j314t}\right)\right]$
Peak value	$10\sqrt{2}$	$120\sqrt{2}$
Frequency	$20 \text{ rad/s} = 3.18 \text{ Hz}$	$314 \text{ rad/s} = 50 \text{ Hz}$
RMS value	10	120
Phase	$-\frac{\pi}{3} = -60^\circ$	$-\frac{\pi}{4} = -45^\circ$
Phasor	$10 e^{-j\pi/3} = 10 \angle -60^\circ$	$120 e^{-j\pi/4} = 120 \angle -45^\circ$

	(e)	(f)
AC waveform	$-50 \sin\left(4t - \frac{\pi}{3}\right)$ $= 35.4\sqrt{2} \cos\left(4t - \frac{\pi}{3} - \frac{\pi}{2} + \pi\right)$ $= \operatorname{Re}\left[(35.4e^{j\pi/6})(\sqrt{2}e^{j4t})\right]$	$0.25 \cos(2t + 100^\circ)$ $= 0.177\sqrt{2} \cos(2t + 1.75)$ $= \operatorname{Re}\left[(0.177e^{j1.75})(\sqrt{2}e^{j2t})\right]$
Peak value	50	0.25
Frequency	4 rad/s = 0.637 Hz	2 rad/s = 0.318 Hz
RMS value	35.4	0.177
Phase	$\frac{\pi}{6} = 30^\circ$	1.75 = 100°
Phasor	$35.4e^{j\pi/6} = 35.4/\underline{30^\circ}$	$0.177e^{j1.75} = 0.177/\underline{100^\circ}$

Q.2

(a)	$\frac{100}{\sqrt{2}} e^{j30^\circ} \text{ V}$	$\operatorname{Re}\left[\left(\frac{100}{\sqrt{2}} e^{j\pi/6}\right)(\sqrt{2}e^{j100\pi t})\right] = 100 \cos\left(314t + \frac{\pi}{6}\right) \text{ V}$
(b)	$115e^{j\pi/3} \text{ V}$	$\operatorname{Re}\left[(115e^{j\pi/3})(\sqrt{2}e^{j100\pi t})\right] = 115\sqrt{2} \cos\left(314t + \frac{\pi}{3}\right) \text{ V}$
(c)	$-0.12e^{-j\pi/4} \text{ A}$	$\operatorname{Re}\left[(-0.12e^{-j\pi/4})(\sqrt{2}e^{j100\pi t})\right] = \operatorname{Re}\left[(e^{j\pi} 0.12e^{-j\pi/4})(\sqrt{2}e^{j100\pi t})\right]$ $= 0.12\sqrt{2} \cos\left(314t + \frac{3\pi}{4}\right) \text{ A}$
(d)	$-0.69/\underline{60^\circ} \text{ A}$	$\operatorname{Re}\left[(-0.69e^{j\pi/3})(\sqrt{2}e^{j100\pi t})\right] = \operatorname{Re}\left[(e^{j\pi} 0.69e^{j\pi/3})(\sqrt{2}e^{j100\pi t})\right]$ $= 0.69\sqrt{2} \cos\left(314t + \frac{4\pi}{3}\right)$ $= 0.69\sqrt{2} \cos\left(314t - \frac{2\pi}{3}\right) \text{ A}$


Q.3 From $v_R(t) = 12\sqrt{2} \cos(2t) \text{ V}$

Frequency = $\omega = 2 \text{ rad/s}$

$$\text{Impedance of capacitor} = \frac{1}{j\omega 0.1} = \frac{1}{j0.2} = -5j\Omega$$

$$\text{Impedance of inductor} = j\omega 2 = 4j\Omega$$

$$V_R = 12e^{j0} = 12$$

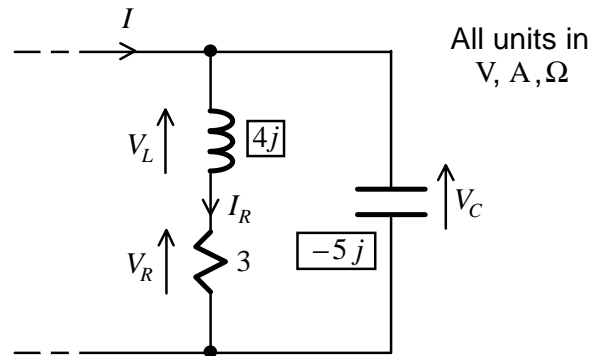


$$I_R = \frac{V_R}{3} = 4 \Rightarrow i_R(t) = 4\sqrt{2} \cos(2t) \text{ A}$$

$$V_L = (4j)I_R = 16j \text{ V} \Rightarrow v_L(t) = 16\sqrt{2} \cos\left(2t + \frac{\pi}{2}\right) \text{ V}$$

$$V_C = V_R + V_L = 12 + 16j$$
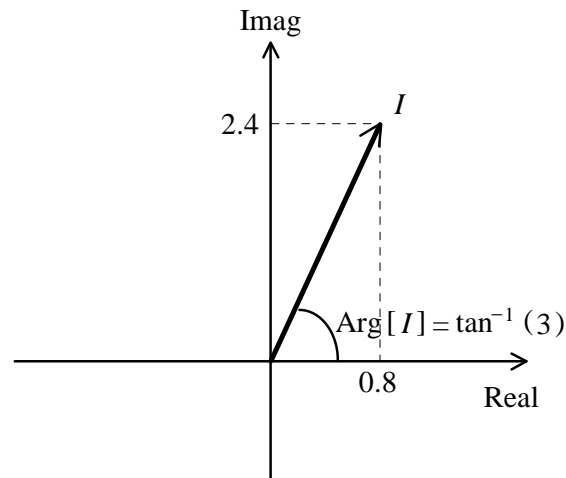
$$I = I_R + \frac{V_C}{-5j} = 4 - \frac{12+16j}{5j} = 4 + 2.4j - 3.2 = 0.8 + 2.4j$$



$$|I| = |0.8 + 2.4j| = \sqrt{0.8^2 + 2.4^2} = 2.53$$

$$\text{Arg}[I] = \text{Arg}[0.8 + 2.4j] = \tan^{-1}\left(\frac{2.4}{0.8}\right) = 1.25$$

$$I = 0.8 + 2.4j = 2.53e^{j1.25} \Rightarrow 2.53\sqrt{2} \cos(2t + 1.25) \text{ A}$$


Q.4

Impedances and phasors

$$v(t) = 50\sqrt{2} \cos(1250t + 30^\circ) \text{ V} \Rightarrow V = 50e^{j30^\circ} \text{ V.}$$

Impedance of inductor = $j(1250)(0.02) = j25\Omega$

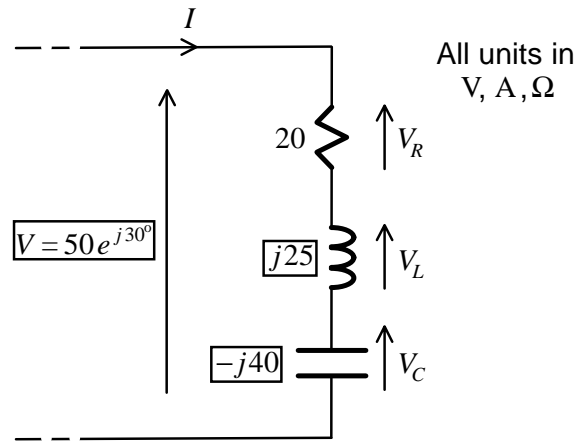Impedance of capacitor = $\frac{1}{j(1250)(0.00002)} = -j40\Omega$



Total impedance = $20 + j25 - j40 = 20 - j15 = \sqrt{20^2 + 15^2} e^{j \tan^{-1}\left(\frac{-15}{20}\right)} = 25e^{-36.9^\circ} \Omega$



$I = \frac{V}{20 + j25 - j40} = \frac{50e^{j30^\circ}}{25e^{-j36.9^\circ}} = 2e^{j66.9^\circ} \text{ A}$

$V_R = 20I = (20)(2e^{j66.9^\circ}) = 40e^{j66.9^\circ} \text{ V}$

$V_L = j25I = (25e^{j90^\circ})(2e^{j66.9^\circ}) = 50e^{j156.9^\circ} \text{ V}$

$V_C = -j40I = (40e^{-j90^\circ})(2e^{j66.9^\circ}) = 80e^{-j23.1^\circ} \text{ V}$

Phasor diagram

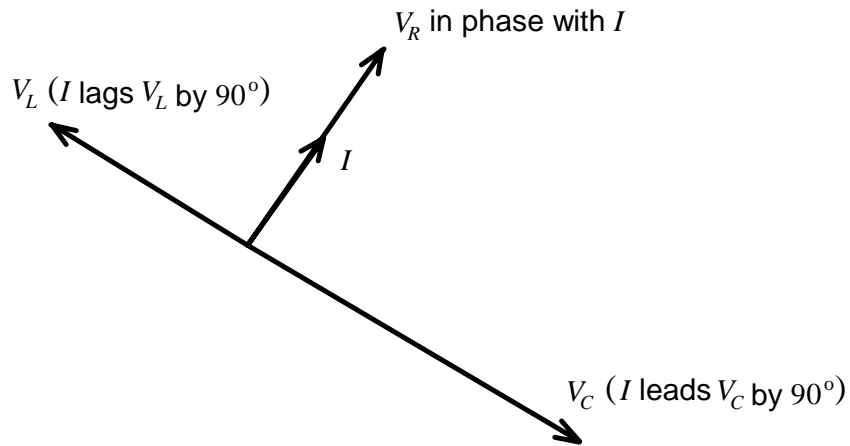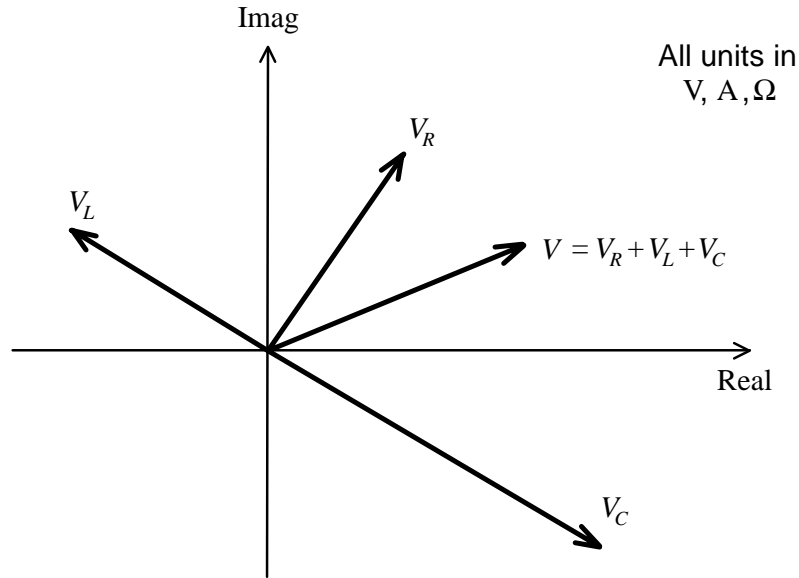

Q.5

Components

The impedances of series RL , RC and LC circuits are

$$Z_{RL} = R + j\omega L = R + j100\pi L$$

$$Z_{RC} = R + \frac{1}{j\omega C} = R - \frac{j}{100\pi C}$$

$$Z_{LC} = j\omega L + \frac{1}{j\omega C} = j\left(100\pi L - \frac{1}{100\pi C}\right)$$

$20 + j30$ must correspond to a series RL circuit with components:

$$R_1 + j100\pi L_1 = 20 + j30 \Rightarrow R_1 = 20\Omega \text{ and } L_1 = \frac{30}{100\pi} = 0.0955\text{H}$$

$10 - j15$ must correspond to a series RC circuit with components:

$$R_2 - \frac{j}{100\pi C_2} = 10 - j15 \Rightarrow R_2 = 10\Omega \text{ and } C_2 = \frac{1}{100\pi(15)} = 212.3 \mu\text{F}$$

Circuit admittance

$$\text{Circuit impedance} = Z = (20 + j30) \parallel (10 - j15) = \frac{1}{\frac{1}{20 + j30} + \frac{1}{10 - j15}}$$

$$\begin{aligned} \text{Circuit admittance} &= \frac{1}{Z} = \frac{1}{20 + j30} + \frac{1}{10 - j15} = \frac{20 - j30}{20^2 + 30^2} + \frac{10 + j15}{10^2 + 15^2} \\ &= 0.0154 - j0.0231 + 0.0308 + j0.0462 = (0.0462 + j0.0231)\Omega^{-1} \end{aligned}$$


Power factor

$$\text{Power factor} = \left\langle \begin{array}{l} \text{value} = \cos[\text{Arg}(I) - \text{Arg}(V)] \\ \text{leading / lagging} = \begin{cases} \text{leading, } \text{Arg}(I) - \text{Arg}(V) > 0 \\ \text{lagging, } \text{Arg}(I) - \text{Arg}(V) < 0 \end{cases} \end{array} \right\rangle$$

$$\text{Arg}(I) - \text{Arg}(V) = \text{Arg}\left(\frac{I}{V}\right) = \text{Arg}\left(\frac{1}{Z}\right) = -\text{Arg}(Z)$$


$$= \text{Arg}(0.0462 + j0.0231) = \tan^{-1}\left(\frac{0.0231}{0.0462}\right) = 0.464$$
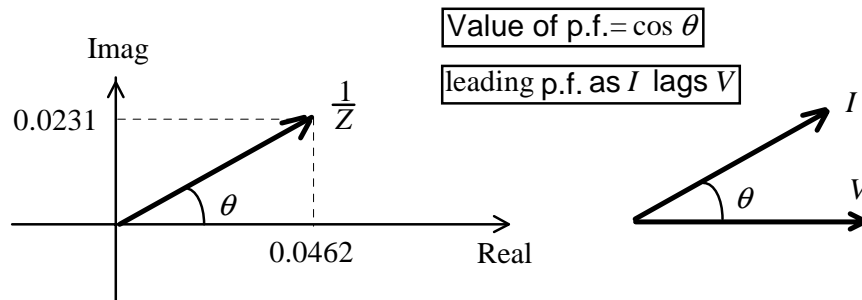
$$\text{Power factor} = \left\langle \begin{array}{l} \text{value} = \cos(0.464) = 0.894 \\ \text{leading / lagging} = \begin{cases} \text{leading, } 0.464 > 0 \\ \text{lagging, } 0.464 < 0 \end{cases} \end{array} \right\rangle = \left\langle \begin{array}{l} 0.894 \\ \text{leading} \end{array} \right\rangle$$



F.6 Analiza Cir El c.a. II

Q.1 Circuit diagram

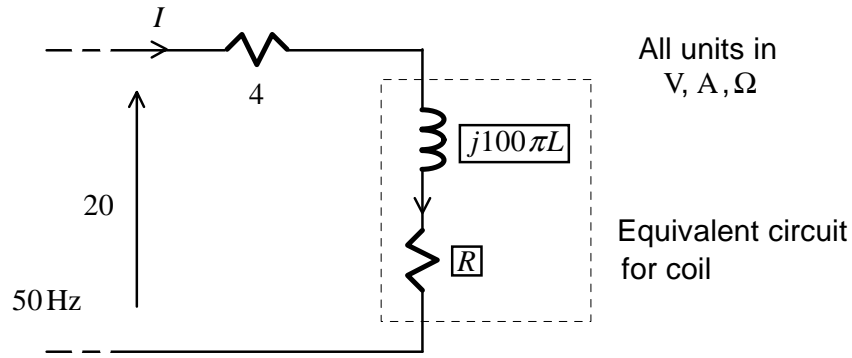

Main equations

$$|\text{Voltage across } 4\Omega| = |4I| = 9 \Rightarrow |I| = \frac{9}{4}$$

$$|\text{Voltage across coil}| = |I(R + j100\pi L)| = 14$$

$$|R + j314L| = \frac{14}{|I|} = 14\left(\frac{4}{9}\right) = 6.222 \Rightarrow R^2 + (314L)^2 = 38.72$$

$$|\text{Supply}| = |I(4 + R + j100\pi L)| = 20$$

$$|4 + R + j314L| = \frac{20}{|I|} = 20\left(\frac{4}{9}\right) = 8.889 \Rightarrow (R+4)^2 + (314L)^2 = 79.01$$

Component values

$$\left[(R+4)^2 + (314L)^2\right] - \left[R^2 + (314L)^2\right] = 79.01 - 38.72$$

$$8R + 16 = 40.29 \Rightarrow R = \frac{40.29 - 16}{8} = 3.04\Omega$$

$$R^2 + (314L)^2 = 38.72 \Rightarrow (314L)^2 = 38.72 - 3.04^2 = 29.48 \Rightarrow L = \frac{\sqrt{29.48}}{314} = 0.0173\text{H}$$

Power and power factor

$$\text{Power absorbed by coil} = |I|^2 R = \left(\frac{9}{4}\right)^2 (3.04) = 15.4\text{ W}$$

$$\text{Power factor} = \left\langle \begin{array}{l} \text{value} = \cos[\text{Arg}(\text{current}) - \text{Arg}(\text{voltage})] \\ \text{leading / lagging} = \begin{cases} \text{leading, } \text{Arg}(\text{current}) - \text{Arg}(\text{voltage}) > 0 \\ \text{lagging, } \text{Arg}(\text{current}) - \text{Arg}(\text{voltage}) < 0 \end{cases} \end{array} \right\rangle$$

$$\text{Arg}(\text{current}) - \text{Arg}(\text{voltage}) = \text{Arg}\left(\frac{\text{current}}{\text{voltage}}\right)$$

$$= \text{Arg}\left(\frac{1}{\text{Impedance}}\right) = -\text{Arg}(\text{Impedance})$$


$$\text{Power factor} = \left\langle \begin{array}{l} \text{value} = \cos[\text{Arg}(\text{impedance})] \\ \text{leading / lagging} = \begin{cases} \text{leading, Arg(impedance)} < 0 \\ \text{lagging, Arg(impedance)} > 0 \end{cases} \end{array} \right\rangle$$

$$\text{Arg(impedance)} = \text{Arg}(R + j314L) = \text{Arg}(3.04 + j314 \times 0.0173)$$


$$= \text{Arg}(7.04 + j5.43) = \tan^{-1}\left(\frac{5.43}{7.04}\right) = 0.657$$

$$\text{Power factor} = \left\langle \begin{array}{l} \text{value} = \cos(0.657) = 0.792 \\ \text{leading / lagging} = \begin{cases} \text{leading, } 0.657 < 0 \\ \text{lagging, } 0.657 > 0 \end{cases} \end{array} \right\rangle = \left\langle \begin{array}{l} 0.792 \\ \text{lagging} \end{array} \right\rangle$$

Q.2 Load current

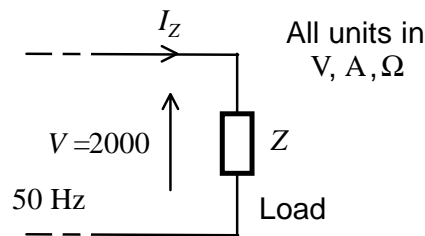

$$\text{Load power factor} = \frac{\text{actual power}}{\text{apparent power}} \Rightarrow 0.5 = \frac{10000}{2000|I_Z|} \Rightarrow |I_Z| = 10 \text{ A}$$

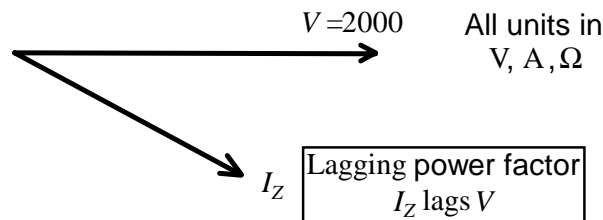


$$\begin{array}{l} 0.5 \text{ lagging} \\ \text{load p.f.} \end{array} \Rightarrow \left\langle \begin{array}{l} \cos[\text{Arg}(I_Z) - \text{Arg}(V)] = 0.5 \\ \text{Arg}(I_Z) - \text{Arg}(V) < 0 \end{array} \right\rangle$$

$$\Rightarrow \left\langle \begin{array}{l} \text{Arg}(I_Z) = \pm \cos^{-1}(0.5) = \pm 1.05 \\ \text{Arg}(I_Z) < 0 \end{array} \right\rangle$$

$$\Rightarrow \text{Arg}(I_Z) = -1.05$$


$$I_Z = |I_Z| e^{j\text{Arg}[I_Z]} = 10 e^{-j1.05} \text{ A}$$

Power factor improvement

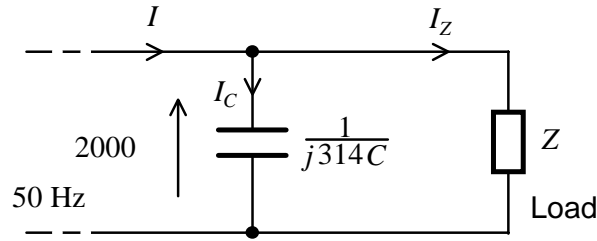

$$I_C = (j314C)(2000) = j628000C$$
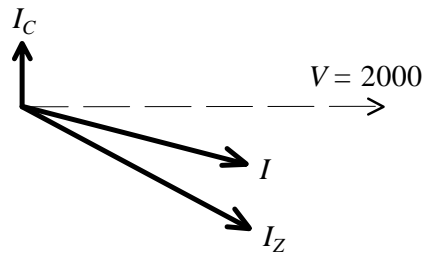
$$I = I_Z + I_C = 10e^{-j1.05} + j628000C = 5 + j(62800C - 8.66)$$



$$\begin{aligned} \text{0.9 lagging overall p.f.} &\Rightarrow \left\langle \begin{aligned} \cos[\text{Arg}(I) - \text{Arg}(V)] = 0.9 \\ \text{Arg}(I) - \text{Arg}(V) < 0 \end{aligned} \right\rangle \Rightarrow \left\langle \begin{aligned} \text{Arg}(I) = \pm 0.451 \\ \text{Arg}(I) < 0 \end{aligned} \right\rangle \end{aligned}$$

$$\Rightarrow \text{Arg}(I) = -0.451 \Rightarrow \tan^{-1}\left(\frac{628000C - 8.66}{5}\right) = -0.451$$

$$\Rightarrow C = \frac{8.66 - 5 \tan(-0.451)}{628000} = 0.0000176 \text{ F} = 17.6 \mu\text{ F}$$

$$\begin{aligned} \text{unity overall p.f.} &\Rightarrow \left\langle \begin{aligned} \cos[\text{Arg}(I) - \text{Arg}(V)] = 1 \\ \text{Arg}(I) - \text{Arg}(V) = 0 \end{aligned} \right\rangle \Rightarrow \text{Arg}(I) = 0 \end{aligned}$$


$$\Rightarrow \tan^{-1}\left(\frac{628000C - 8.66}{5}\right) = 0 \Rightarrow C = \frac{8.66}{628000} = 0.0000138 \text{ F} = 13.8 \mu\text{ F}$$

$$\begin{aligned} \text{0.8 leading overall p.f.} &\Rightarrow \left\langle \begin{aligned} \cos[\text{Arg}(I) - \text{Arg}(V)] = 0.8 \\ \text{Arg}(I) - \text{Arg}(V) > 0 \end{aligned} \right\rangle \Rightarrow \left\langle \begin{aligned} \text{Arg}(I) = \pm 0.644 \\ \text{Arg}(I) > 0 \end{aligned} \right\rangle \end{aligned}$$

$$\Rightarrow \text{Arg}(I) = 0.644 \Rightarrow \tan^{-1}\left(\frac{628000C - 8.66}{5}\right) = 0.644$$

$$\Rightarrow C = \frac{8.66 + 5 \tan(0.644)}{628000} = 0.0000078 \text{ F} = 7.8 \mu\text{ F}$$

Q.3 Power

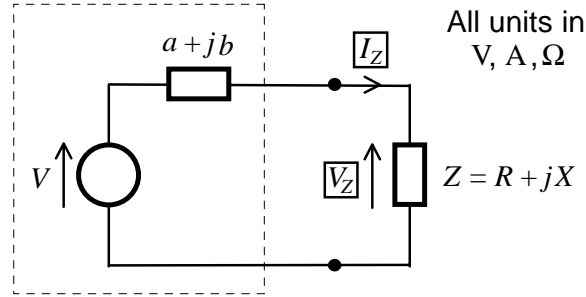

Electrical system

$$I_Z = \frac{V}{(a + jb) + (R + jX)} = \frac{V}{(a + R) + j(b + X)}$$

$$V_Z = I_Z(R + jX)$$

$$\begin{aligned} \text{Power absorbed} = p &= \text{Re}[I_Z^* V_Z] = \text{Re}[|I_Z|^2 (R + jX)] \\ &= |I_Z|^2 \text{Re}[R + jX] = R|I_Z|^2 \\ &= R \left| \frac{V}{(a + R) + j(b + X)} \right|^2 = \frac{R|V|^2}{(a + R)^2 + (b + X)^2} \end{aligned}$$

Maximum power transfer

For maximum p , the denominator should be as small as possible. As the numerator does not depend on X and the smallest value for $(b + X)$ is 0, maximum power will be absorbed if

$$X = -b$$

so that

$$p = \frac{|V|^2 R}{(a + R)^2}$$

Differentiating:

$$\frac{dp}{dR} = |V|^2 \left[\frac{1}{(a + R)^2} - \frac{2R}{(a + R)^3} \right] = |V|^2 \left[\frac{a - R}{(a + R)^3} \right]$$


Thus, maximum p occurs when

$$R = a$$



and the maximum power transferable is

$$p = \frac{|V|^2 R}{(R + R)^2} = \frac{|V|^2}{4R} = \frac{|V|^2}{4a} \text{ W}$$

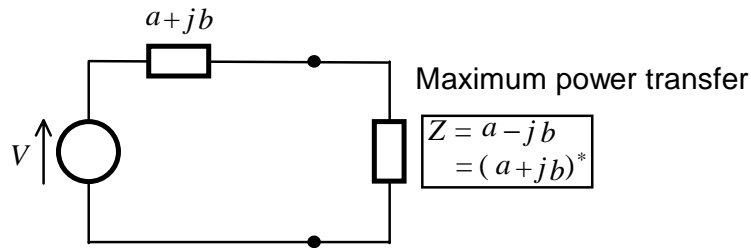
In general, maximum power transfer occurs when the load impedance is equal to the conjugate of the Thevenin's or Norton's impedance. When this occurs, the total impedance is purely resistive and the current and voltage in the circuit are in phase:



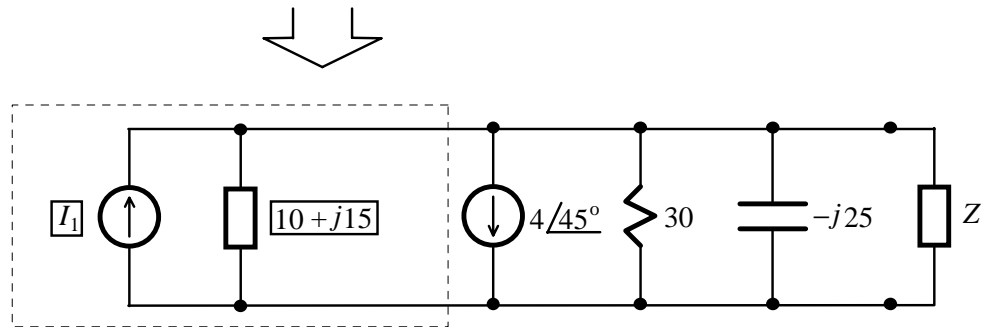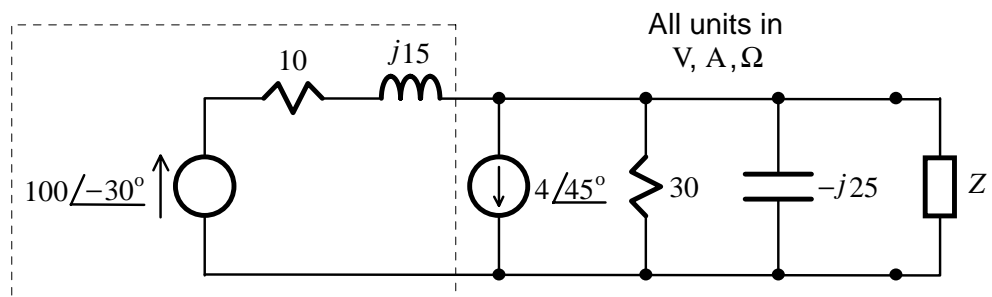Q.4 Norton's and Thevenin's equivalent circuit


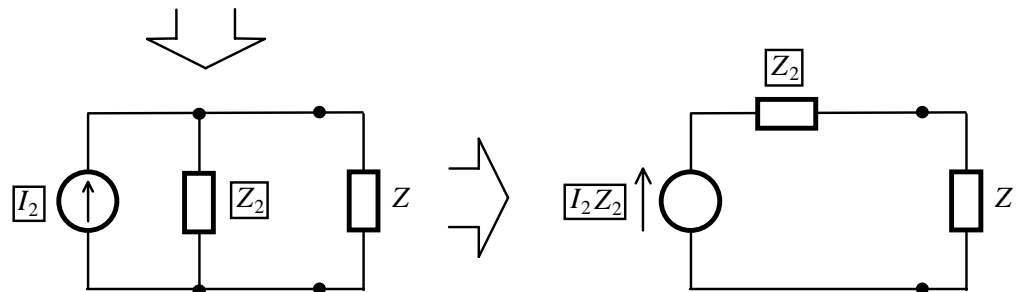
$$I_1 = \frac{100e^{-j30^\circ}}{10 + j15} = \frac{100e^{-j30^\circ}}{18e^{j56.3^\circ}} = 5.55e^{-j86.3^\circ} = 0.358 - j5.54$$




$$Z_2 = -j25 \parallel 30 \parallel (10 + j15) = \frac{1}{\frac{1}{-j25} + \frac{1}{30} + \frac{1}{10 + j15}} = \frac{1}{\frac{1}{-j25} + \frac{1}{30} + \frac{10 - j15}{10^2 + 15^2}}$$

$$= \frac{1}{0.0641 - j0.00615} = \frac{1}{0.0644e^{-j5.48^\circ}} = 155e^{j5.48^\circ}$$

$$I_2 = 0.359 - j5.55 - 4e^{j45^\circ} = -2.47 - j8.36 = 8.72e^{-j106^\circ}$$

Maximum power transfer

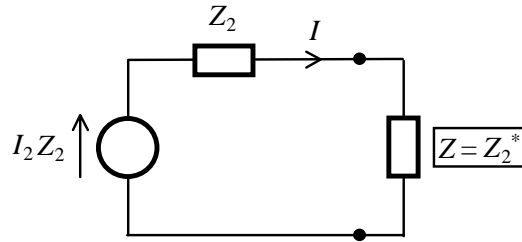From the previous problem, this occurs when



$$Z = Z_2^* = (15.5e^{j5.48^\circ})^* = 15.5e^{-j5.48^\circ}$$


$$\text{Total impedance} = Z + Z_2 = Z_2^* + Z_2 = 15.5e^{j5.48^\circ} + 15.5e^{-j5.48^\circ} = 2[15.5\cos(5.48^\circ)]$$

$$I = \frac{I_2 Z_2}{(Z + Z_2)} = \frac{8.72e^{-j106^\circ} 15.5e^{j5.48^\circ}}{2[15.5\cos(5.48^\circ)]} = \frac{8.72e^{-j101^\circ}}{2\cos(5.48^\circ)}$$

Thus, the maximum power transferable is

$$\begin{aligned} \text{Re}[I^*(IZ)] &= |I|^2 \text{Re}[Z_2^*] \\ &= \left| \frac{8.72e^{-j101^\circ}}{2\cos(5.48^\circ)} \right|^2 \text{Re}[15.5e^{-j5.48^\circ}] = \left| \frac{8.72}{2\cos(5.48^\circ)} \right|^2 15.5\cos(5.48^\circ) \\ &= \frac{8.72^2 \times 15.5}{4\cos(5.48^\circ)} = 297 \text{ W} \end{aligned}$$

Q.5

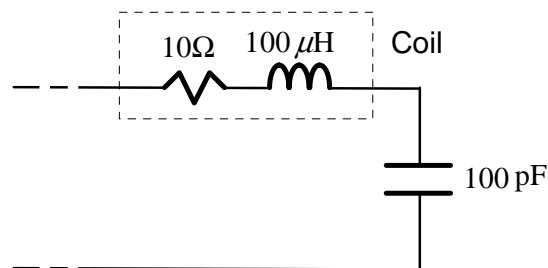

$$\text{Resonant frequency} = \frac{1}{2\pi\sqrt{(100 \times 10^{-6})(100 \times 10^{-12})}} = 1.59 \text{ MHz}$$


$$Q \text{ factor} = \frac{2\pi(1.59 \times 10^6)(100 \times 10^{-6})}{10} = 100$$

Since the Q factor is large, the circuit is bandpass in nature with

$$3\text{dB cutoff frequencies} \approx 1.59 \left(1 \pm \frac{1}{200} \right) \text{ MHz}$$

$$\text{Bandwidth} \approx \frac{1.59 \times 10^6}{100} = 15.9 \text{ kHz}$$

Q.6

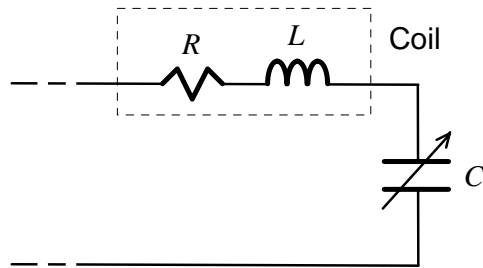

$$C = 20 \dots 500 \text{ pF} \Rightarrow \text{resonant frequency} = \frac{1}{2\pi\sqrt{L(500 \times 10^{-12})}} \dots \frac{1}{2\pi\sqrt{L(20 \times 10^{-12})}}$$

$$= \frac{7.12}{\sqrt{L}} \dots \frac{35.6}{\sqrt{L}} \text{ kHz}$$

For the lowest tunable frequency to be 666 kHz:

$$666 = \frac{7.12}{\sqrt{L}} \Rightarrow L = \left(\frac{7.12}{666}\right)^2 = 0.114 \text{ mH}$$

The highest tunable frequency is then

$$\frac{35.6}{\sqrt{L}} = \frac{35.6}{\sqrt{0.114 \times 10^{-3}}} = 3.42 \text{ MHz}$$