

CAP.6.

B) CIRCUITE MONOFAZATE IN REGIM SINUSOIDAL

6.6. (R) Pentru a se determina inductivitatea L si rezistenta R a unei bobine se masoara valoarea efectiva a tensiunii U la bornele bobinei si a curentului care o strabate, la doua frecvente diferite f_1 si f_2 ale tensiunii sinusoidale aplicate si anume:

$$U_1=60 \text{ V}; I_1=10 \text{ A}; f_1=50 \text{ Hz}$$

$$U_2=60 \text{ V}; I_2=6 \text{ A}; f_2=100 \text{ Hz}$$

Sa se calculeze inductivitatea si rezistenta R a bobinei.

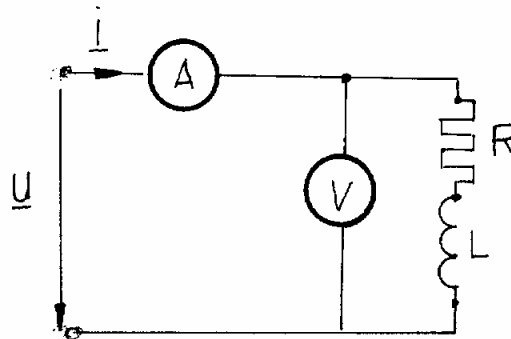


Fig.6.6

Rezolvare: Modulul impedantei complexe echivalente a bobinei este in cele doua cazuri:

$$\frac{U_1}{I_1} = \sqrt{R^2 + \omega_1^2 \cdot L^2}; \omega_1 = 2 \cdot \pi f_1$$

$$\frac{U_2}{I_2} = \sqrt{R^2 + \omega_2^2 \cdot L^2}$$

$$\text{Se obtine sistemul } \begin{cases} R^2 + 10^4 \cdot \pi^2 \cdot L^2 = 36 \\ R^2 + 4 \cdot 10^4 \cdot \pi^2 \cdot L^2 = 100 \end{cases} \Rightarrow \begin{matrix} L = 14,7 \cdot 10^{-3} \text{ H} \\ R = 3,84 \Omega \end{matrix}$$

6.7. (R) Un rezistor cu rezistenta $R=100 \Omega$ si un condensator de capacitate $C=2\mu\text{F}$ sunt conectate in serie. Tensiunea la bornele condensatorului are valoarea instantanee:

$$u_c=10 \cdot \sin 5000 t$$

Sa se calculeze tensiunea la bornele rezistorului u_R si la bornele intregului circuit u , precum si puterea instantanee absorbita.

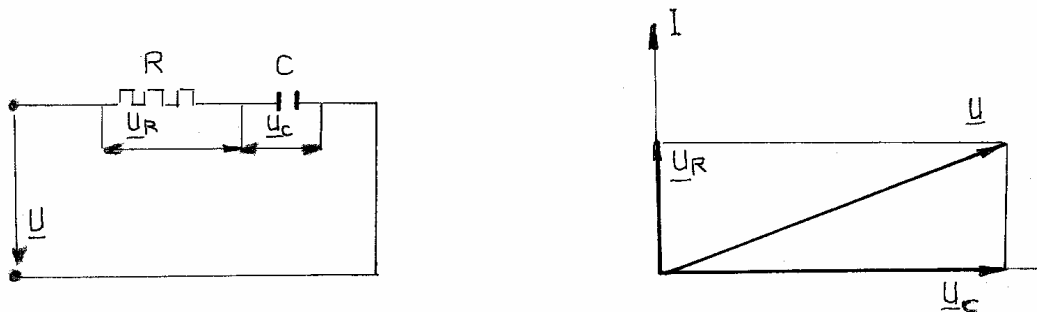


Fig. 6.7

Rezolvare: $u_c = 10 \cdot \sin 5000 t$

Reprezentarea in complex simplificat a tensiunii u_c este:

$$\underline{U}_c = 10 / \sqrt{2} \cdot e^{j0}$$

Impedanta complexa este:

$$\underline{Z}_c = \frac{1}{j\omega C} = 10^2 \cdot j = 10^2 \cdot e^{-j\pi/2}$$

Curentul care strabate circuitul este in complex:

$$\underline{I} = \frac{\underline{U}_c}{\underline{Z}_c} = \frac{10 \cdot e^{j0}}{\sqrt{2} \cdot 10^2 \cdot e^{-j\pi/2}} = \frac{1}{10 \cdot \sqrt{2}} \cdot e^{j\pi/2}$$

iar in valoare instantanee:

$$i = \sqrt{2} \cdot \frac{1}{10 \cdot \sqrt{2}} \cdot \sin(\omega t + \pi/2)$$

Tensiunea la bornele intregului circuit este:

$$\underline{U} = \underline{U}_R + \underline{U}_c = j \cdot 10 / \sqrt{2} + 10 / \sqrt{2} = 10 / \sqrt{2} (i + j) = 10 \cdot e^{j\pi/4}$$

si deci:

$$u = \sqrt{2} \cdot 10 \cdot \sin(\omega t + \pi/4)$$

Puterea instantanee absorbita de circuit este:

$$p = u \cdot i = \sqrt{2} \cdot 10 \cdot \sin(\omega t + \pi/4) \cdot [1/10 \cdot \sin(\omega t + \pi/2)]$$

Cum $\sin a \cdot \sin b = \frac{1}{2} [\cos(a - b) - \cos(a + b)]$, rezulta:

$$p = \frac{\sqrt{2}}{2} \cdot \left[\frac{\sqrt{2}}{2} + \sin\left(2\omega t + \frac{\pi}{4}\right) \right] = 0,5 + 0,707 \cdot \sin\left(10^4 t + \frac{\pi}{4}\right)$$

6.8. (R) O bobina de parametrii $R=10 \Omega$ si $L=10 \text{ mH}$ conectata in serie cu un condensator de capacitate $C=50 \mu\text{F}$ este parcursa de curentul $i=0,2 \sin(1000t)$.

Sa se calculeze valorile instantanee ale tensiunilor u , u_R , u_L , u_C si sa se efectueze bilantul puterilor.

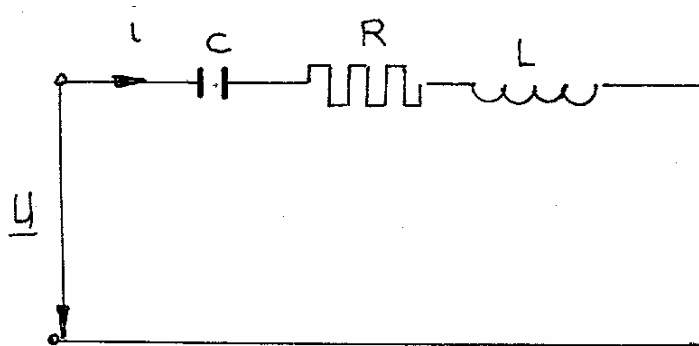


Fig. 6.8

Rezolvare: Curentul care strabate circuitul este:

$$i = I_M \sin \omega t = \sqrt{2} \cdot I \cdot \sin \omega t, \text{ unde:}$$

$$I_M = 0,2 \text{ A}; I = \frac{0,2}{\sqrt{2}} = 0,142 \text{ A}; \omega = 1000 \text{ rad/s}$$

Reprezentarea in complex simplificat a curentului este:

$$\underline{I} = 0,142 e^{j \cdot 0}$$

Reactantele inductiva si capacitiva ale circuitului sunt:

$$\underline{X}_L = \omega L = 10 \Omega; \underline{X}_C = -\frac{U}{\omega C} = -20 \Omega$$

Impedanta complexa a circuitului este:

$$\underline{Z} = R + j \left(\omega L - \frac{1}{\omega C} \right) = 10 - j \cdot 10 = 10 \cdot \sqrt{2} \cdot e^{-j \cdot \pi/4}$$

Tensiunile sunt:

$$\underline{U} = \underline{Z} \cdot \underline{I} = 2 \cdot e^{-j \cdot \pi/4} = \sqrt{2}(1 - j)$$

$$\underline{U}_R = R \cdot \underline{I} = 10 \cdot 0,142 \cdot e^{j \cdot 0} = 1,42$$

$$\underline{U}_L = j \cdot \omega L \cdot \underline{I} = 1,42 \cdot e^{j \pi/2} = j \cdot 1,42$$

$$\underline{U}_C = \frac{1}{j \omega C} \cdot \underline{I} = 2,84 \cdot e^{-j \cdot \pi/2} = -j \cdot 2,84$$

Verificare:

$$\underline{U} = \underline{U}_R + \underline{U}_L + \underline{U}_C = \sqrt{2}(1 - j)$$

Valorile instantanee ale tensiunilor sunt:

$$u = \sqrt{2} \cdot 2 \cdot \sin(\omega t - \pi/4)$$

$$u_R = \sqrt{2} \cdot 1,42 \cdot \sin \omega t$$

$$u_L = \sqrt{2} \cdot 1,42 \cdot \sin(\omega t + \pi/2)$$

$$u_C = \sqrt{2} \cdot 2,84 \cdot \sin(\omega t - \pi/2)$$

Puterea aparenta complexa este:

$$\underline{S} = \underline{U} \cdot \underline{I}^* = 0,284 \cdot e^{-j \cdot \pi/4} = (0,2 - j \cdot 0,2) \text{ VA}$$

$$\underline{S} = P + j \cdot Q$$

$$P = R \cdot I^2 = 10 \cdot 0,142^2 = 0,2 \text{ W}$$

$$Q = X_L \cdot I^2 + X_C \cdot I^2 = -0,2 \text{ Var}$$

Bilantul puterilor este verificat.

6.9. (R) La variatii ale parametrilor receptorului R_1 , X_1 nu se poate determina semnul unghiului φ_1 numai cu aparatele din fig.6.9 (ampermetru, voltmetru si wattmetru). In acest scop se recurge la o masuratoare suplimentara cu o bobina conectata in serie. Aparatele conectate in circuit indica:

1. Intrerupatorul k inchis: $U=100 \text{ V}; I=10 \text{ A}; P=300 \text{ W}$.

2. Intrerupatorul k deschis: $U=100 \text{ V}; I=12,5 \text{ A}; P=625 \text{ W}$.

Sa se calculeze R_1 , X_1 , Z_1 ale receptorului si R_2 , X_2 , Z_2 ale bobinei introduse.

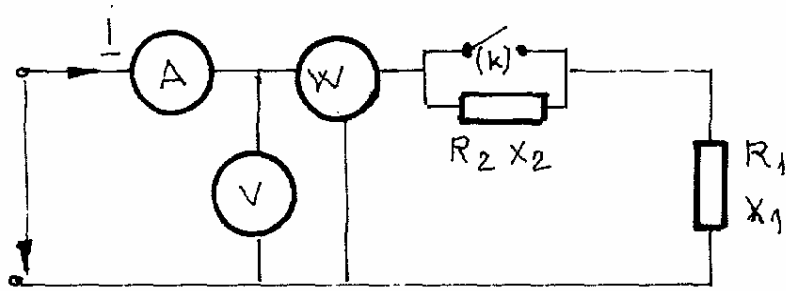


Fig. 6.9

Rezolvare:

1. Intrerupatorul k inchis:

Impedanta complexa a circuitului are modulul:

$$Z = \frac{U}{I} = \frac{100}{10} = 10\Omega$$

si argumentul:

$$\varphi = \arccos \frac{P}{U \cdot I} = \arccos(0,3) = 72^{\circ}30'$$

$$\text{Deci: } \underline{Z}_1 = 10 \cdot e^{\pm j \cdot 72^{\circ}30' \cdot \pi : 180} = 3 \pm j \cdot 9,55$$

2. Intrerupatorul k deschis:

$$Z_1 = \frac{U}{I} = \frac{100}{12,5} = 8\Omega$$

$$\varphi = \arccos \frac{P}{U \cdot I} = \arccos(0,5) = 60^{\circ}20'$$

$$\underline{Z} = 8 \cdot e^{j \cdot 60^{\circ}20' \cdot \pi : 180} = 4 + j \cdot 6,96$$

Impedanta complexa echivalenta este:

$$\underline{Z} = \underline{Z}_1 + \underline{Z}_2 \text{ de unde:}$$

$$\underline{Z}_2 = \underline{Z} - \underline{Z}_1 = 4 + j \cdot 6,96 - 3 \pm j \cdot 9,55 = \begin{cases} 1 - j \cdot 2,59 \\ 1 + j \cdot 16,51 \end{cases}$$

Se stie ca receptorul \underline{Z}_2 este inductiv, deci:

$$\underline{Z}_2 = 1 + j \cdot 16,51$$

ceea ce conduce la concluzia ca receptorul \underline{Z}_1 este capacitiv:

$$\underline{Z}_1 = 3 - j \cdot 9,55 = 10 \cdot e^{-j \cdot 72^{\circ}30' \cdot \pi : 180}$$

Schema circuitului devine:

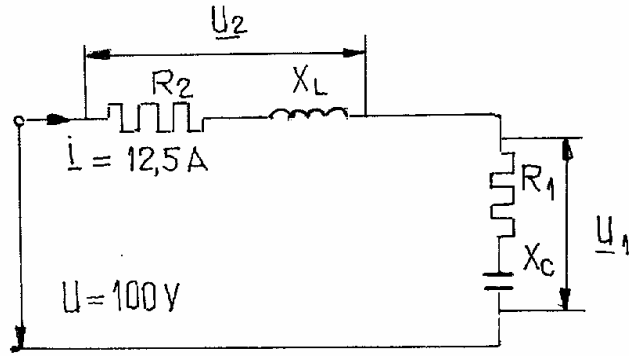


Fig. 6.9.1

6.10 (R) Pentru circuitul din fig.6.10 se cunosc: $e_1(t)=18\sqrt{2} \cdot \sin \omega t$, $e_2(t)=12 \cdot \sqrt{2} \cdot \cos(\omega t - \pi)$; $R_1=3\Omega$; $\omega L_1=4\Omega$; $\omega L_1'=1\Omega$; $\frac{1}{\omega C_1}=5\Omega$; $R_2=2\Omega$; $\omega L_2=4\Omega$; $\frac{1}{\omega C_2}=5\Omega$; $\omega L_3=3\Omega$; $\frac{1}{\omega C_3}=4\Omega$; $\omega L_{11}=\omega L_{23}=1\Omega$.

Sa se determine valorile instantanee ale curentilor din laturi si sa se verifice bilantul puterilor.

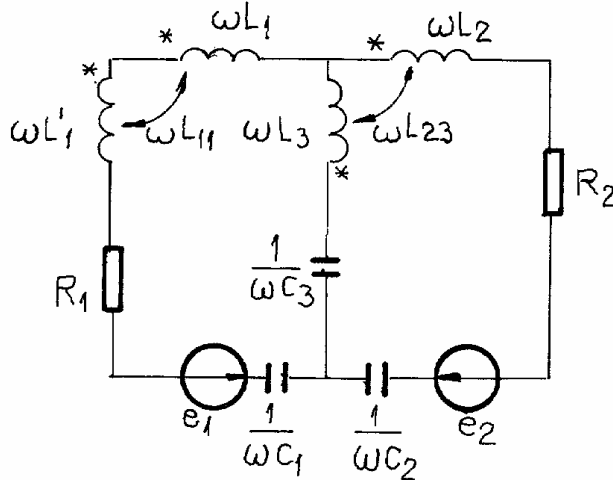


Fig. 6.10

Rezolvare:

Se aplica metoda teoremelor lui Kirchhoff sub forma complexa directa. Cu:

$$e_1(t) = 18 \cdot \sqrt{2} \cdot \sin \omega t \Leftrightarrow \underline{E} = 18 \cdot e^{j0} = 18 \text{ v}$$

$$e_2(t) = 12 \cdot \sqrt{2} \cdot \cos(\omega t - \pi) = 12 \cdot \sqrt{2} \cdot \sin(\omega t - \pi/2) \Leftrightarrow$$

$$\underline{E}_2 = 12 \cdot e^{-j \cdot \pi/2} = -j \cdot 12 \text{ V se poate realiza urmatoarea schema in complex:}$$

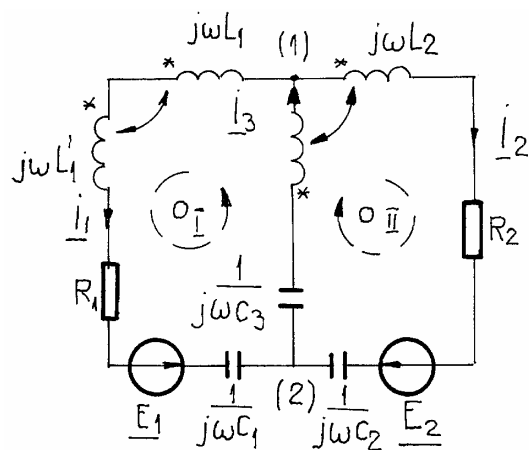


Fig. 6.10.1

Cu sensurile adoptate in figura 6.10.1 si considerând nodul (2) de referinta, rezulta:

$$-I_1 - I_2 + I_3 = 0$$

$$\left[R_1 + j \left(\omega L_1 + \omega L_1' - \frac{1}{\omega C_1} \right) \cdot I_1 - 2j\omega L_{11} \cdot I_1 + j \left(\omega L_3 - \frac{1}{\omega C_3} \right) \cdot I_3 + j\omega L_{23} \cdot I_2 = E_1 \right]$$

$$\cdot I_3 + j\omega L_{23} \cdot I_2 = E_1$$

$$R_2 + j \left(\omega L_2 - \frac{1}{\omega C_2} \right) \cdot I_2 + j \left(\omega L_3 - \frac{1}{\omega C_3} \right) \cdot I_3 +$$

$$+ j \cdot \omega L_{23} \cdot I_3 + j \cdot \omega L_{23} I_2 = E_2$$

Sau numeric:

$$I_3 = I_1 + I_2$$

$$(3 - j \cdot 2) I_1 + j \cdot I_2 - j \cdot I_3 = 18$$

$$2 \cdot I_2 = j \cdot I_2$$

cu solutiile: $I_1 = 3(1 + j) = 3\sqrt{2} \cdot e^{j\pi/4} \text{ A}$; $I_2 = -j \cdot 6 = 6 \cdot e^{-j\pi/2} \text{ A}$ si

$I_3 = 3(1 - j) = 3 \cdot \sqrt{2} \cdot e^{-j\pi/4} \text{ A}$, carora le corespund:

$$i_1(t) = 6 \cdot \sin(\omega t + \pi/4) \text{ A}; i_2(t) = 6 \cdot \sqrt{2} \cdot \sin(\omega t - \pi/2) \text{ A};$$

$$i_3(t) = 6 \cdot \sin(\omega t - \pi/4) \text{ A}$$

Aplicând ecuatia de bilant a puterilor se obtine:

$$\underline{S}_g = \underline{E}_1 \cdot \underline{I}_1^* + \underline{E}_2 \cdot \underline{I}_2^* = 18 \cdot 3(1 - j) + (-j \cdot 12) \cdot j \cdot 6 = 126 - j \cdot 54, \text{ adica:}$$

$P_g = 126 \text{ W}$; $Q_g = -54 \text{ VAR}$, respectiv:

$$P_R + j \cdot Q_X = R_1 \cdot I_1^2 + R_2 \cdot I_2^2 + j \left[\left(\omega L_1 + \omega L_1' - \frac{1}{\omega C_1} \right) \cdot I_1^2 + \right. \\ \left. + \left(\omega L_2 - \frac{1}{\omega C_2} \right) \cdot I_2^2 + \left(\omega L_3 - \frac{1}{\omega C_3} \right) \cdot I_3^2 - 2 L_{11} \cdot I_1 \cdot I_1 \cdot \cos(\gamma_1 - \gamma_1) + \right. \\ \left. + 2\omega L_{23} \cdot I_2 \cdot I_3 \cdot \cos(\gamma_2 - \gamma_3) \right] = 126 - j \cdot 54, \text{ adica:}$$

$$P_R=126 \text{ W}; Q_X=-54 \text{ VAR}$$

Cum $P_g=P_R$, $Q_g=Q_X$, arata ca rezultatele obtinute sunt corecte.

6.11 (R) Pentru circuitul din fig.6.11 se cunosc:

$$\underline{E}_1 = 4 \cdot \sqrt{2} \cdot e^{j\pi/4} = 4(1+j)\text{V}; \quad \underline{I}_g = 2 \cdot e^{j^0} = 2\text{A}; \quad R_1=2\Omega; \quad \omega L_1 = 6\Omega;$$

$$\frac{1}{\omega C_1} = 10\Omega; \quad \omega L_2 = 8\Omega; \quad \frac{1}{\omega C_2} = 6\Omega; \quad \omega L_{12} = 2\Omega.$$

Se cer valorile instantanee ale curentilor din laturi si sa se verifice bilantul puterilor.

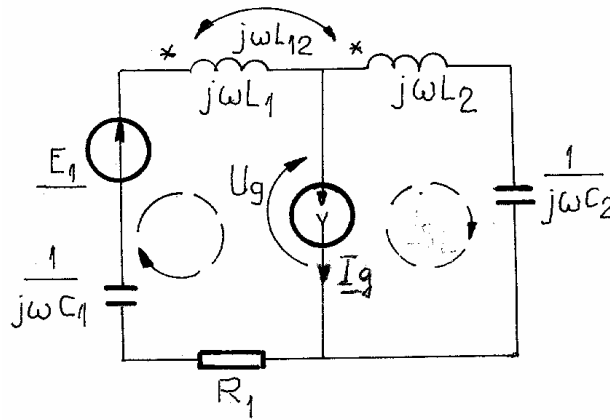


Fig. 6.11

Rezolvare: Se aplica metoda teoremelor lui Kirchoff sub forma complexa directa. Cu sensurile adoptate in fig.6.11, rezulta:

$$\underline{I}_1 - \underline{I}_2 = \underline{I}_g$$

$$\left(R_1 + j\omega L_1 + \frac{1}{j\omega C_1} \right) \underline{I}_1 + j\omega L_{12} \cdot \underline{I}_2 - \underline{U}_g = \underline{E}_1$$

$$j\omega L_{12} \underline{I}_1 + \left(j\omega L_2 + \frac{1}{j\omega C_2} \right) \cdot \underline{I}_2 + \underline{U}_g = 0$$

sau numeric:

$$\begin{cases} \underline{I}_1 - \underline{I}_2 = 2 \\ (2 - j \cdot 4) \cdot \underline{I}_1 + j \cdot 2 \cdot \underline{I}_2 - \underline{U}_g = 4(1+j) \\ j \cdot 2 \cdot \underline{I}_1 + j \cdot 2 \cdot \underline{I}_2 + \underline{U}_g = 0 \end{cases}$$

cu solutiile: $\underline{I}_1 = 2(2+j) = 2 \cdot \sqrt{2} \cdot e^{j \arctg 1/2} \text{ A};$

$$\underline{I}_2 = 2(1+j) = 2 \cdot \sqrt{2} \cdot e^{j\pi/4} \text{ A};$$

$$\underline{U}_g = 4(2 - j \cdot 3) = 4 \cdot \sqrt{130} \cdot e^{-j \arctg 3/2} \text{ V, carora le corespund:}$$

$$i_1(t) = 2 \cdot \sqrt{10} \cdot \sin(\omega t + 26^{\circ}34' \cdot \pi/180) \text{ A};$$

$$i_2(t) = 4 \cdot \sin(\omega t + \pi/4) \text{ A};$$

$$u_g(t) = 4 \cdot \sqrt{26} \cdot \sin(\omega t - 56^{\circ} 10' \cdot \pi / 180) \text{ V.}$$

Verificarea bilantului puterilor:

$$\underline{S}_g = \underline{E}_1 \cdot \underline{I}_1^* + \underline{U}_g \cdot \underline{I}_g^* = 4(1+j) \cdot (2-j) + 4 \cdot (2-j) \cdot 3 \cdot 2 = 40 - j \cdot 16$$

adica: $P_g=40\text{W}$; $Q_g=-16\text{VAr}$.

$$P_R + j \cdot Q_X = R_1 \cdot I_1^2 + j \left(\omega L_1 - \frac{1}{\omega C_1} \right) \cdot I_1^2 + \left(\omega L_2 - \frac{1}{\omega C_2} \right) \cdot I_2^2 +$$

$\omega L_{12} (\underline{I}_1 \cdot \underline{I}_2^* + \underline{I}_2 \cdot \underline{I}_1^*) = 40 - j \cdot 16$, adica: $P_R=40 \text{ W}$; $Q_X=-16 \text{ VAr}$ deci rezultatele obtinute sunt corecte.