

## DECODERS I

Decoders are combinational logic circuits that activate one or more outputs, according to code applied at its inputs. Their applications are memory addressing digital display, data multiplexing, etc.

### 1. Address decoder with enable inputs

This type of decoder is used for memory addressing in microprocessor systems. The circuit activates a single output corresponding to the input code. The activation occurs only if the enable inputs are activated (the circuit is selected).

Such a very used circuit is 74LS138 (fig.1), whose truth table is shown below:

 


Figure 1

$E_1$	$\overline{E_2}$	$\overline{E_3}$	$C$	$B$	$A$	$\overline{Y_7}$	$\overline{Y_6}$	$\overline{Y_5}$	$\overline{Y_4}$	$\overline{Y_3}$	$\overline{Y_2}$	$\overline{Y_1}$	$\overline{Y_0}$	Remarks
0	X	X	X	X	X	1	1	1	1	1	1	1	1	circuit is off
X	1	X	X	X	X	1	1	1	1	1	1	1	1	circuit is off
X	X	1	X	X	X	1	1	1	1	1	1	1	1	circuit is off
1	0	0	0	0	0	1	1	1	1	1	1	1	0	$Y_0$ is active
1	0	0	0	0	1	1	1	1	1	1	1	0	1	$Y_1$ is active
1	0	0	0	1	0	1	1	1	1	1	0	1	1	$Y_2$ is active
1	0	0	0	1	1	1	1	1	1	0	1	1	1	$Y_3$ is active
1	0	0	1	0	0	1	1	1	0	1	1	1	1	$Y_4$ is active
1	0	0	1	0	1	1	1	0	1	1	1	1	1	$Y_5$ is active
1	0	0	1	1	0	1	0	1	1	1	1	1	1	$Y_6$ is active
1	0	0	1	1	1	0	1	1	1	1	1	1	1	$Y_7$ is active

The circuit has 3 inputs (A, B, C) for the code word (address):

$$\overline{Y}_i = 0 \leftarrow i \Big|_Z = CBA \Big|_B = C \cdot 2^2 + B \cdot 2^1 + A \cdot 2^0 \Big|_Z$$

and 3 inputs for circuit selection (circuit enable): one active on logic 1 ( $E_1$ ) and 2 active on logic 0 ( $\overline{E_2}$  and  $\overline{E_3}$ ). The circuit is selected (active) when all three enable inputs are active ( $E_1$  is active AND  $\overline{E_2}$  is active AND  $\overline{E_3}$  is active). Those three variables can be replaced with a single one  $E = E_1 \cdot \overline{E_2} \cdot \overline{E_3}$  for simplifying the synthesis. The truth table can be rewritten for 4 input variables.

**2. BCD to decimal decoder**

In practice we frequently find situations when we need to decode a BCD (Binary to decimal) code – for example displaying on Nixie tubes. This is similar with the address decoder, except it has ten outputs. The truth table is shown below.

D	C	B	A	$\overline{Y_9}$	$\overline{Y_8}$	$\overline{Y_7}$	$\overline{Y_6}$	$\overline{Y_5}$	$\overline{Y_4}$	$\overline{Y_3}$	$\overline{Y_2}$	$\overline{Y_1}$	$\overline{Y_0}$	Remarks
0	0	0	0	1	1	1	1	1	1	1	1	1	0	Y <sub>0</sub> is active
0	0	0	1	1	1	1	1	1	1	1	1	0	1	Y <sub>1</sub> is active
0	0	1	0	1	1	1	1	1	1	1	0	1	1	Y <sub>2</sub> is active
0	0	1	1	1	1	1	1	1	1	0	1	1	1	Y <sub>3</sub> is active
0	1	0	0	1	1	1	1	1	0	1	1	1	1	Y <sub>4</sub> is active
0	1	0	1	1	1	1	1	0	1	1	1	1	1	Y <sub>5</sub> is active
0	1	1	0	1	1	1	0	1	1	1	1	1	1	Y <sub>6</sub> is active
0	1	1	1	1	1	0	1	1	1	1	1	1	1	Y <sub>7</sub> is active
1	0	0	0	1	0	1	1	1	1	1	1	1	1	Y <sub>8</sub> is active
1	0	0	1	0	1	1	1	1	1	1	1	1	1	Y <sub>9</sub> is active
1	0	1	0	1	1	1	1	1	1	1	1	1	1	outputs off
1	0	1	1	1	1	1	1	1	1	1	1	1	1	outputs off
1	1	0	0	1	1	1	1	1	1	1	1	1	1	outputs off
1	1	0	1	1	1	1	1	1	1	1	1	1	1	outputs off
1	1	1	0	1	1	1	1	1	1	1	1	1	1	outputs off
1	1	1	1	1	1	1	1	1	1	1	1	1	1	outputs off

The circuit works only with BCD input code. We can consider the outputs for the input combinations greater than 9 (1001) as being don't care in order to obtain a simpler circuit. The above table is complete and no output will be active for the codes greater than 9. The circuit will be more complicated in this case.

**3. Works to do in the lab**

Complete the following sheet according to the indications.

**LAB SHEET**

1. Starting from the reduced truth table complete the VK diagrams below and extract the minimized equations for the 8 outputs.

EC \ BA	00	01	11	10
00				
01				
11				
10				

$\overline{Y}_0 =$

EC \ BA	00	01	11	10
00				
01				
11				
10				

$\overline{Y}_2 =$

EC \ BA	00	01	11	10
00				
01				
11				
10				

$\overline{Y}_4 =$

EC \ BA	00	01	11	10
00				
01				
11				
10				

$\overline{Y}_6 =$

EC \ BA	00	01	11	10
00				
01				
11				
10				

$\overline{Y}_1 =$

EC \ BA	00	01	11	10
00				
01				
11				
10				

$\overline{Y}_3 =$

EC \ BA	00	01	11	10
00				
01				
11				
10				

$\overline{Y}_5 =$

EC \ BA	00	01	11	10
00				
01				
11				
10				

$\overline{Y}_7 =$

2. From the equations deduced at 1st requirement, build the circuit of the address decoder with logic gates:

3. Introduce the circuit in MaxPlusII and simulate it. Draw the waveforms resulted from simulation below. Determine the delay time between in and out.

Waveforms:

