

## COMPARATOARE NUMERICE

Digital comparators are combinational logic circuits that detect the relative value of 2 binary numbers. Such circuit has a symbol like in figure 1 and has  $2 \times n$  inputs for the 2 numbers and 3 outputs:  $A > B$ ,  $A = B$  și  $A < B$ .

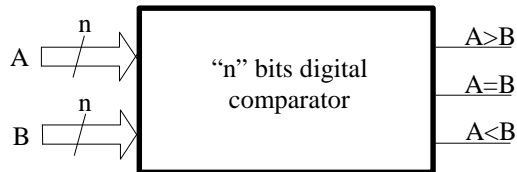


Figure 1

### 1. 1 bit digital comparator

This circuit allows comparing 2 numbers of 1 bit each, indicating on the 3 outputs the relation between them:  $>$ ,  $=$ ,  $<$ . This is a particular case of the above

 


Figure 2

case, with  $n=1$ . The symbol and the truth table of the circuit are presented in figure 2.

The output  $y_i$  is logic 1 when the input numbers respect the relation corresponding to the output, in the rest being logic 0. The associated VK diagrams are the following:

	$B_i$	0	1
$A_i$	0	0	1
0	0	0	1
1	0	0	0

$$y_1 = \bar{A}_i \cdot B_i$$

	$B_i$	0	1
$A_i$	0	1	0
0	0	1	0
1	0	0	1

$$y_2 = \bar{A}_i \cdot \bar{B}_i + A_i \cdot B_i = A_i \oplus B_i$$

	$B_i$	0	1
$A_i$	0	0	0
0	0	0	0
1	0	1	0

$$y_3 = A_i \cdot \bar{B}_i$$

**LAB no. 7**

From the equations deduced above we can build the circuit from figure 3.

 


Figure 3

**2. 2 bits digital comparator**

Using two 1 bit comparators we can build a 2 bits comparator. The numbers to be compared have the decimal equivalents:

$$A = A_0 \cdot 2^0 + A_1 \cdot 2^1$$

$$B = B_0 \cdot 2^0 + B_1 \cdot 2^1$$

Comparing binary numbers give the same results as comparing their decimal equivalents. The comparison follows the logic diagram shown in figure 4.

The comparison starts with the most significant  $A_1$  and  $B_1$ . If  $A_1 > B_1$  or  $A_1 < B_1$  we can deduce that  $A > B$  and respectively  $A < B$ , no matter what are the bits  $A_0$  and  $B_0$ .

If  $A_1 = B_1$ , for establishing the relation between the 2 numbers, we have to look for the relation between  $A_0$  and  $B_0$ . If  $A_0 = B_0$  the output  $Y_2$  ( $A = B$ ) will be activated. If  $A_0 > B_0$  or  $A_0 < B_0$  then  $A > B$  or respectively  $A < B$  and the corresponding output will be activated.

This reasoning can be extended for many bits. Another alternative assume to build the truth table and using the VK diagrams to minimize the logic functions and make the schematic with logic gates. This will be used in the following.

 



Figure 4

### 3. Lab work

Print the Lab sheet below and complete it according to the indications.

**LAB SHEET**

 1. Introduce the schematic from figure 3 in MaxPlus II and simulate the circuit. Draw the waveforms obtained from simulation respecting the delays. Write the delay times and the logic value on the waveforms. Compare the results with the truth table.



2. Complete the the 2 bits digital comparator truth table.

$B_1$	$B_0$	$A_1$	$A_0$	$Y_{A>B}$	$Y_{A=B}$	$Y_{A<B}$
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			

**LAB no. 7**

3. Synthesize the 2 bits comparator using the VK diagrams.

$B_1B_0$	00	01	11	10
$A_1A_0$				
00				
01				
11				
10				

$B_1B_0$	00	01	11	10
$A_1A_0$				
00				
01				
11				
10				

$y_{A>B} =$

$B_1B_0$	00	01	11	10
$A_1A_0$				
00				
01				
11				
10				

$y_{A=B} =$

$y_{A<B} =$

4. Implement the 2 bits comparator with logic gates and draw it below.

5. Simulate the 2 bits comparator in MaxPlusII and draw the waveforms respecting the delays. Write the delay and the logic states on the waveforms.

